

ASSEMBLY Programming

Logic Design

Dr Jeff Drobman

website → drjeffsoftware.com/classroom.html

email → jeffrey.drobman@csun.edu

Index

- ❖ Logic → slide 3
- ❖ Transistors to Gates → slide 13
- ❖ Arithmetic → slide 19
- ❖ AMD Catalog of Analog (Linear) → slide 31
- ❖ Digital MSI: ALU → slide 35
- ❖ Digital MSI: PIC, Mux/Dec → slide 40
- ❖ Logic Minimize → slide 54
- ❖ Memory (RAM) → slide 62
- ❖ Sequential Logic → slide 67
- ❖ Logic: Multi/Div → slide 78
- ❖ Logic Timing (AC) → slide 97
- ❖ State Machines (FSM) → slide 103
- ❖ Computer Logic Boards → slide 105

Section



Logic

Logic

Relational Operators	
<	less than
<=	less than or equal to
>	greater than
>=	greater than or equal to
==	equal to
!=	not equal

any type → boolean

Logical Operators	
&&	short circuit AND
	short circuit OR
!	NOT
^	exclusive OR

boolean → boolean

```
if (x <= y+3) && x > 2 || _FLAG == true
```

`_FLAG == true ⇔ _FLAG`
`_FLAG == false ⇔ !_FLAG`

- ❖ AND has 2 uses:
 - 1) Mask (1 lets in)
 - 2) Filter (0 keeps out)
- ❖ XOR has 2 uses:
 - 1) Bit complement/toggle
 - 2) Bit equal



Chapters in this Volume

Ch. 1 - Numeration Systems

Ch. 2 - Binary Arithmetic

Ch. 3 - Logic Gates

Ch. 4 - Switches

Ch. 5 - Electromechanical Relays

Ch. 6 - Ladder Logic

Ch. 7 - Boolean Algebra

Ch. 8 - Karnaugh Mapping ➤ *K-maps*

Ch. 9 - Combinational Logic Functions

Ch. 10 - Multivibrators

Ch. 11 - Sequential Circuits

Ch. 12 - Shift Registers

Ch. 13 - Digital-Analog Conversion




Ch. 14 - Digital Communication

Ch. 15 - Digital Storage (Memory)

Logic Comic Book

Manga Guide

   https://nostarch.com/download/MangaGuidetoMicroprocessors_sample_Chapter2.pdf



THIS IS A LABELED DIAGRAM OF THE INSIDE OF THIS CHIP.



Truth Tables

OR

X	Y	$X \ \ Y$
0	0	0
0	1	1
1	0	1
1	1	1

AND

X	Y	$X \ \&\& \ Y$
0	0	0
0	1	0
1	0	0
1	1	1

XOR

	X	Y	$X \ \wedge \ Y$
pass	0	0	0
	0	1	1
flip	1	0	1
	1	1	0

↑ control
↑ data

INclusive

- ❖ AND has 2 uses:
 - 1) Mask (1 lets in)
 - 2) Filter (0 keeps out)
- ❖ XOR has 2 uses:
 - 1) Bit complement/toggle
 - 2) Bit equal

EXclusive

Bit-wise Operations

Appendix G

p. 751

NEW

Operator	Name	Example	Result
&	Bitwise AND	11101 & 00111	00101
	Bitwise OR	00010 11000	11010
^	Bitwise XOR	00111 ^ 11111	11000
~	1's complement	00111100	11000011
<<	Left shift (*2 ⁿ)	10101010 << 2	10101000
>>	Right shift, arith SE	10101011 >> 2	11101010
>>>	Right shift, logical	10101011 >>> 2	00101010

bit flip

*2ⁿ


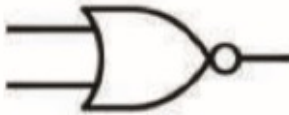

Integer types only

Compound Logic Gates

Manga Guide

OTHER BASIC GATES (NAND, NOR, AND XOR)



OKAY, LET'S TAKE A
LOOK AT NAND, NOR,
AND XOR* GATES NEXT.


NAND	NOR	XOR
		

Compound Logic: NAND

Manga Guide

NAND GATE (LOGIC INTERSECTION COMPLEMENT GATE)

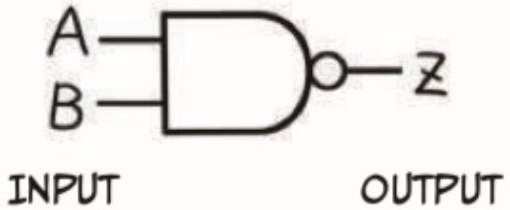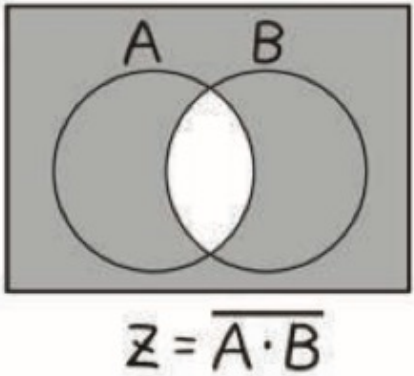SYMBOL	TRUTH TABLE	VENN DIAGRAM															
	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Z</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	Z	0	0	1	0	1	1	1	0	1	1	1	0	 <p>$Z = \overline{A \cdot B}$</p>
A	B	Z															
0	0	1															
0	1	1															
1	0	1															
1	1	0															

 

Logic Gates: Polarity

DeMorgan's Law

Manga Guide

DE MORGAN'S THEOREM

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$



Logic Gates: Polarity

DeMorgan's Law

Manga Guide



That's it! It also means that we can use De Morgan's laws to show our circuits in different ways. Using this technique, it's easy to simplify schematics when necessary.



Section



Transistors Make Gates

Transistors to Computers

— **Quora** —

If computers are really just many (billions) of on/off switches, how do they perform operations?



Jeff Drobman, Lecturer at California State University, Northridge (2016-present)

Answered just now


via a multi-level hierarchy of digital logic. transistors are combined to form logic "gates" of simple logic functions (AND, OR, NOT). the gates are combined to form more complex functions such as decoders, ALUs, and multiplexers. these functional blocks are then combined further into ever more complex logic blocks such as EU's and then CPU cores. also, random logic implements the ICU as an FSM which includes pipelining. besides logic, computers have "storage" in the form of registers and memory (at up to 4 levels) via DRAM and SRAM cells formed from transistors (and a capacitor).

P → N → C MOS

Device/Xtor
Physical
Level


Inverter/Gates

Complementary
CMOS
INVERTER

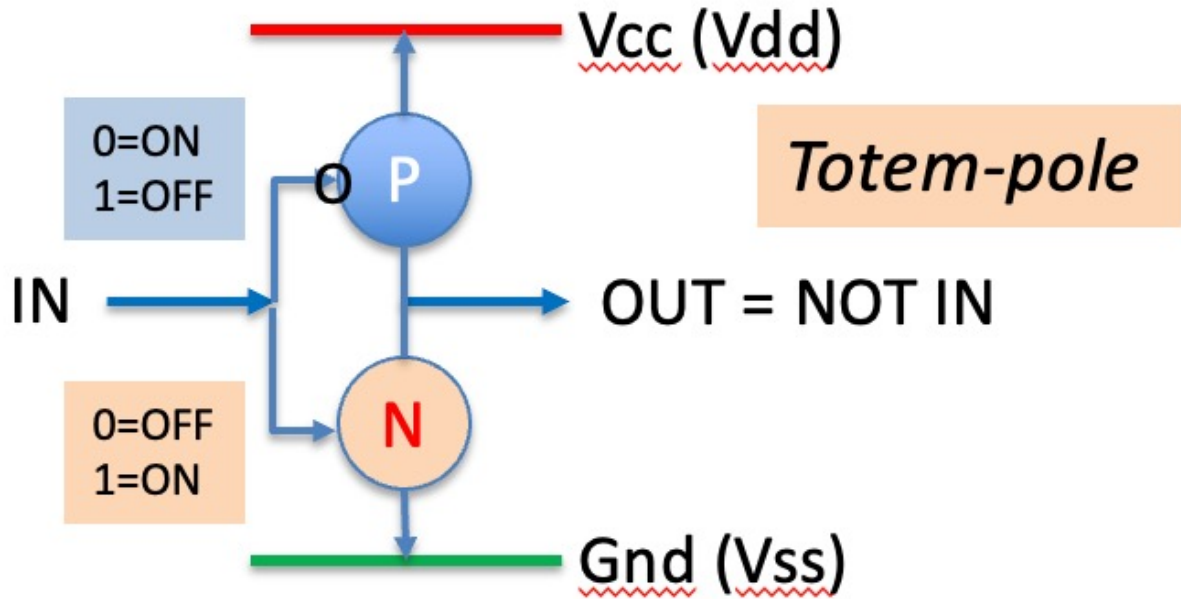


MOS Gates


MOSFET

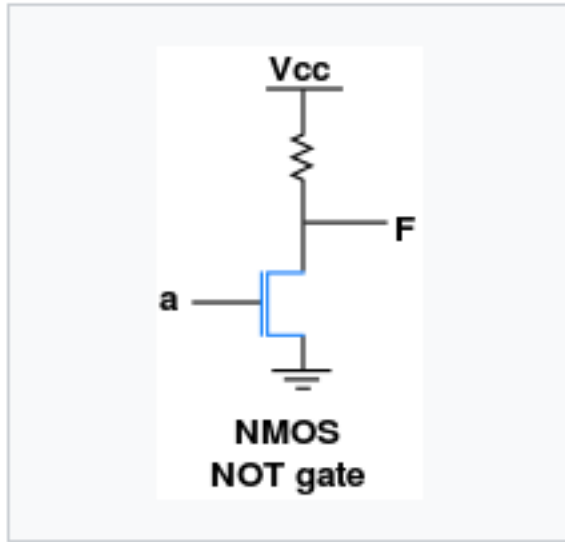

NMOS inverter

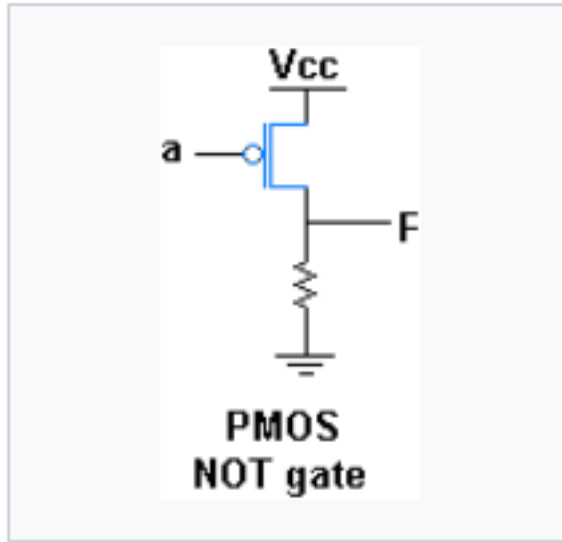

PMOS inverter

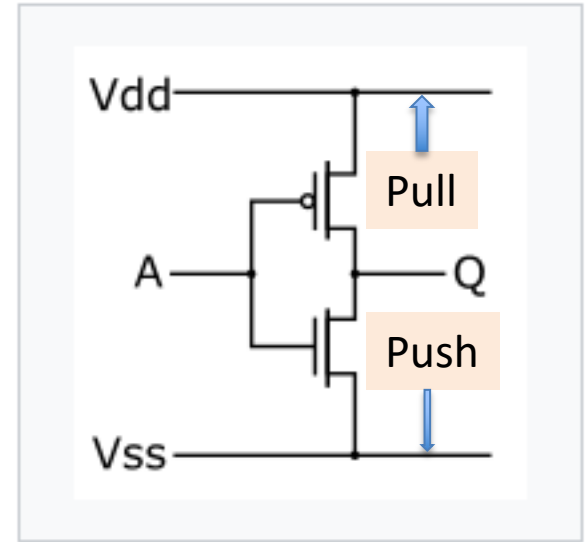


Static CMOS inverter

CMOS

P/N Totem pole

Push-Pull


NOT

 

Logic Gates: AND, OR


AND

SERIES

 



OR

PARALLEL

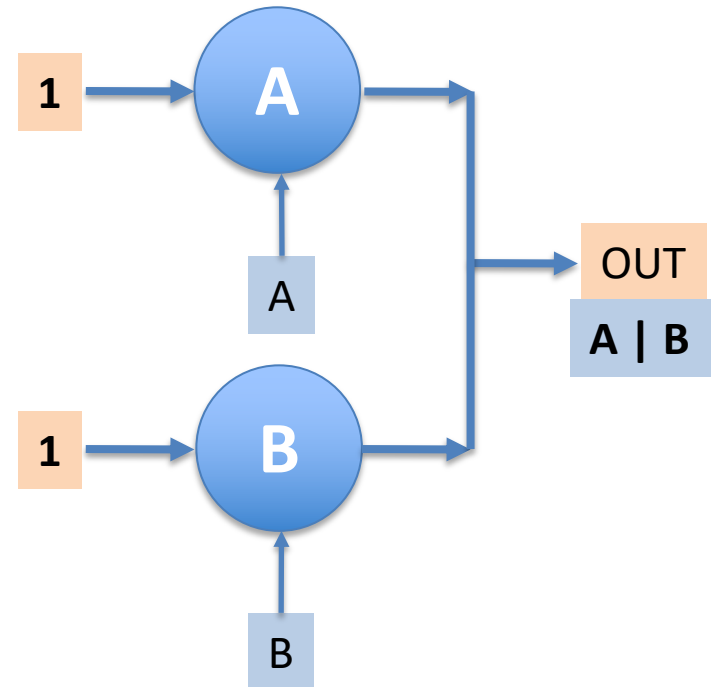


CMOS Gates

MOSFET

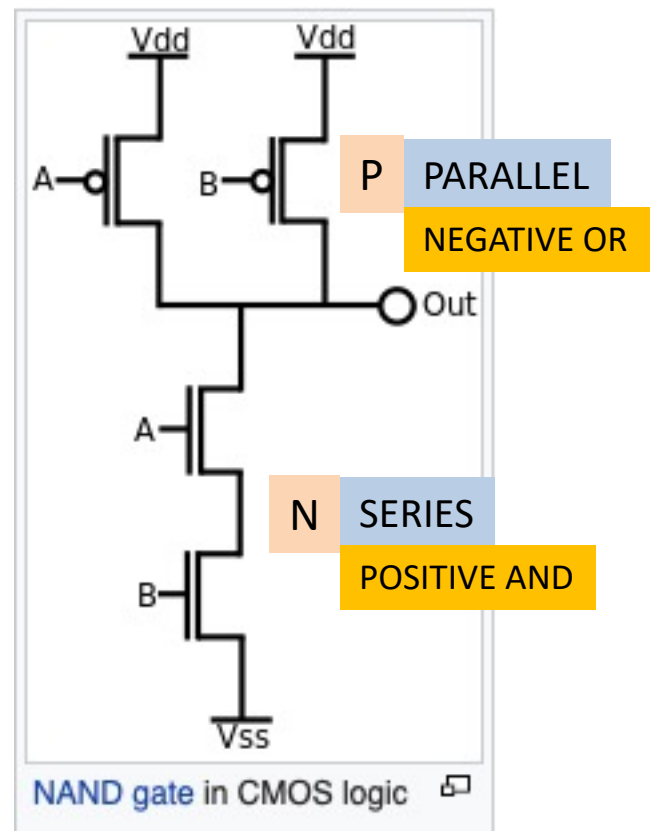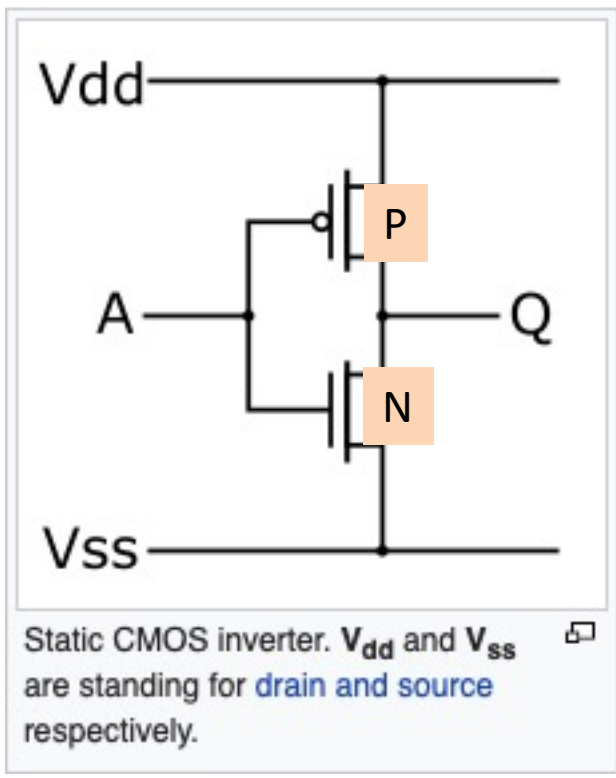

NOT

 

NAND



Section



Arithmetic



ALU Ops

MARS




<code>add \$t1,\$t2,\$t3</code>	Addition with overflow : set \$t1 to (\$t2 plus \$t3)
<code>add.d \$f2,\$f4,\$f6</code>	Floating point addition double precision : Set \$f2 to double-precision floating p
<code>add.s \$f0,\$f1,\$f3</code>	Floating point addition single precision : Set \$f0 to single-precision floating p
<code>addi \$t1,\$t2,-100</code>	Addition immediate with overflow : set \$t1 to (\$t2 plus signed 16-bit immediate)
<code>addiu \$t1,\$t2,-100</code>	Addition immediate unsigned without overflow : set \$t1 to (\$t2 plus signed 16-bit
<code>addu \$t1,\$t2,\$t3</code>	Addition unsigned without overflow : set \$t1 to (\$t2 plus \$t3), no overflow
<code>and \$t1,\$t2,\$t3</code>	Bitwise AND : Set \$t1 to bitwise AND of \$t2 and \$t3
<code>andi \$t1,\$t2,100</code>	Bitwise AND immediate : Set \$t1 to bitwise AND of \$t2 and zero-extended 16-bit im

Adders

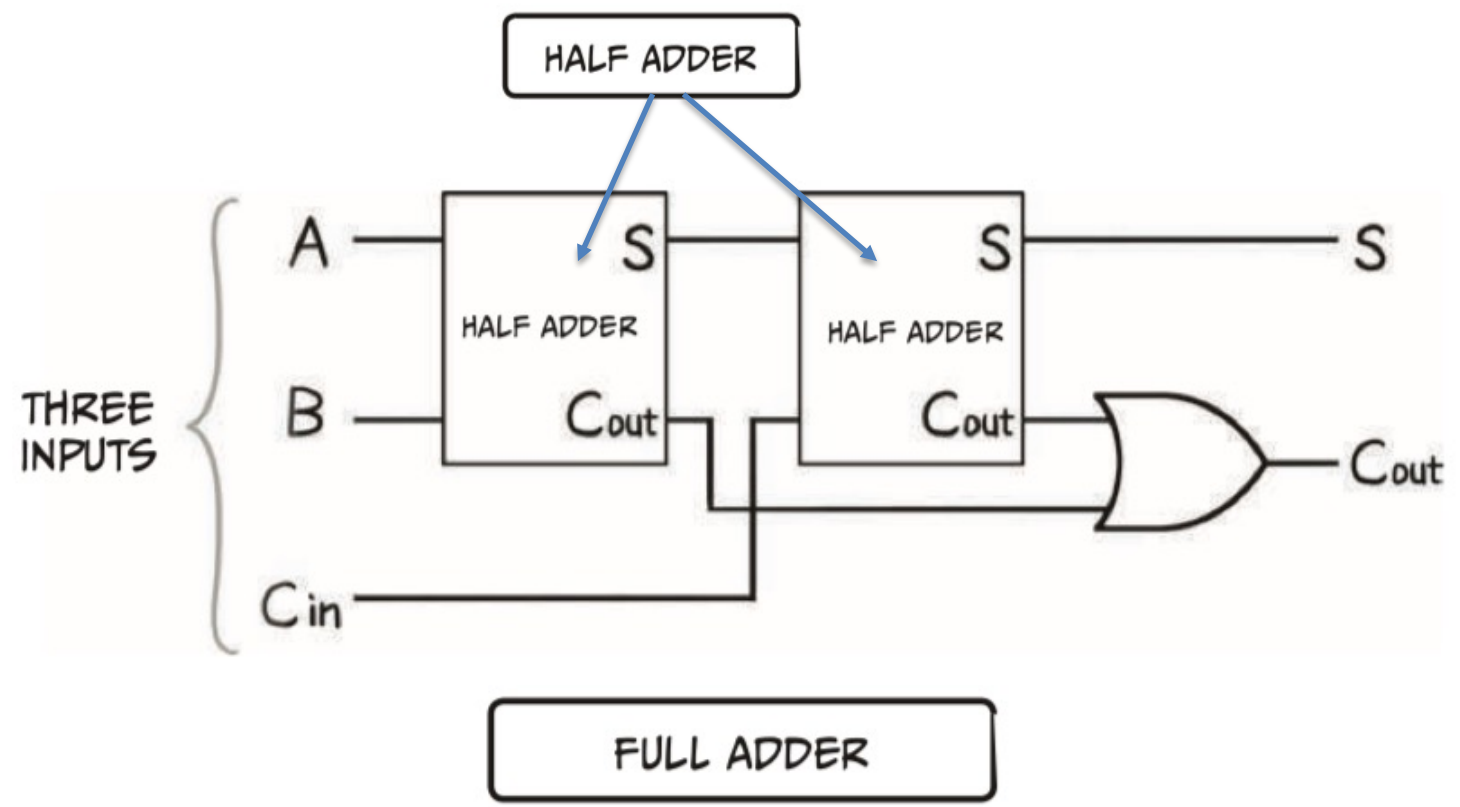 

Adders

 Full Adder in Digital Logic GeeksforGeeks




Inputs			Outputs	
A	B	C - IN	Sum	C - Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Adders


Implementation of Full Adder using Half Adders

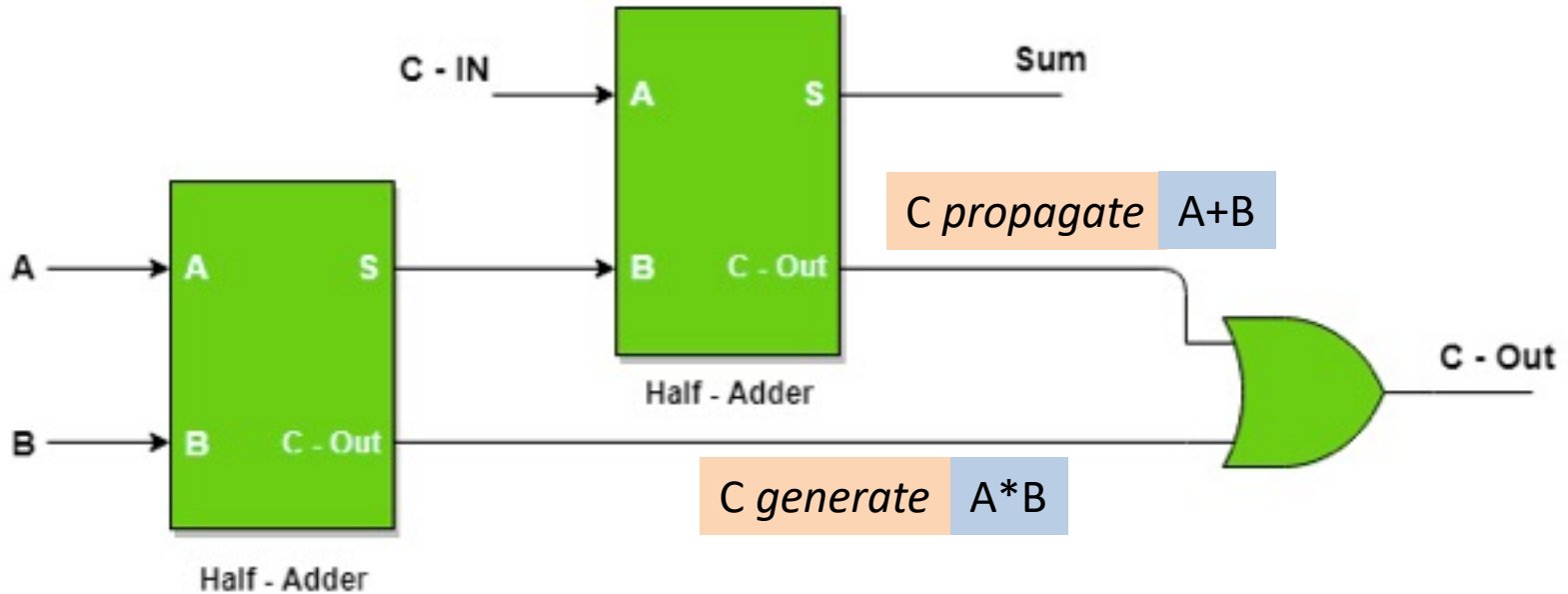2 Half Adders and a OR gate is required to implement a Full Adder.



Adders

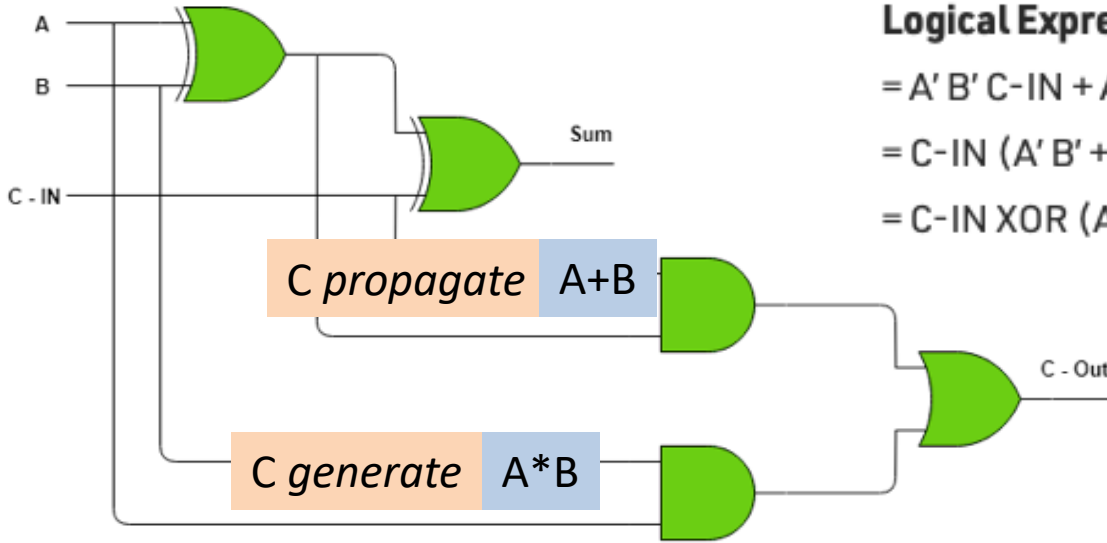Therefore $C_{OUT} = AB + C \cdot IN$ (A EX - OR B)




Full Adder logic



Logical Expression for SUM:

$$\begin{aligned}
 &= A' B' C \cdot IN + A' B C \cdot IN' + A B' C \cdot IN' + A B C \cdot IN \\
 &= C \cdot IN (A' B' + A B) + C \cdot IN' (A' B + A B') \\
 &= C \cdot IN \text{ XOR } (A \text{ XOR } B)
 \end{aligned}$$

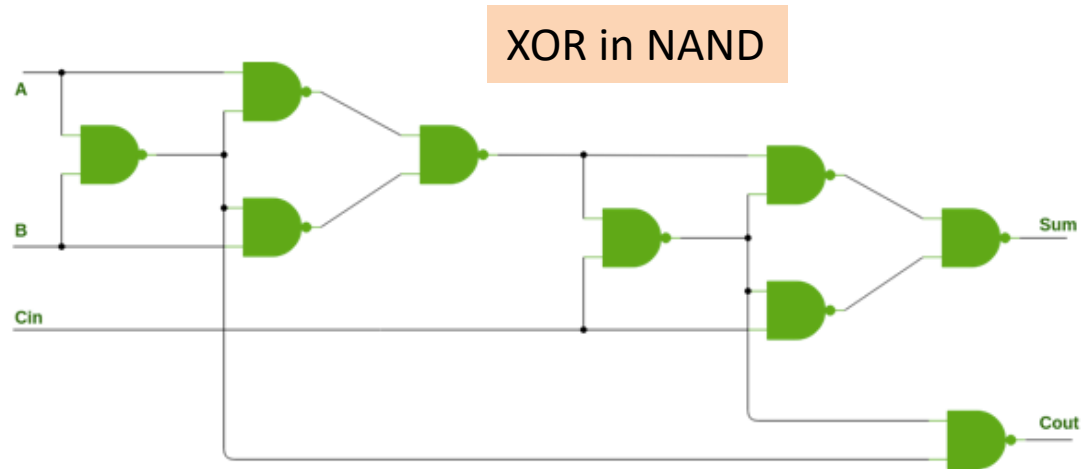Implementation of Full Adder using NAND gates:




Adders: Ripple Carry

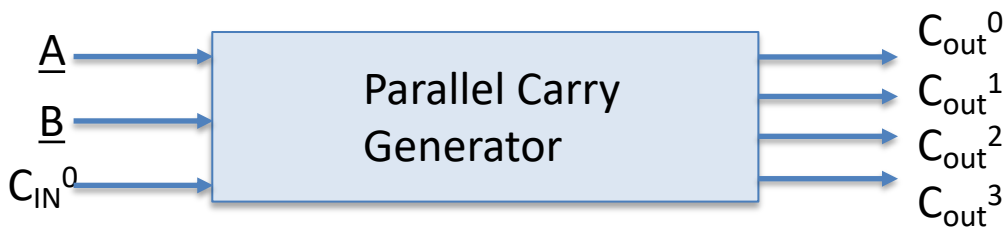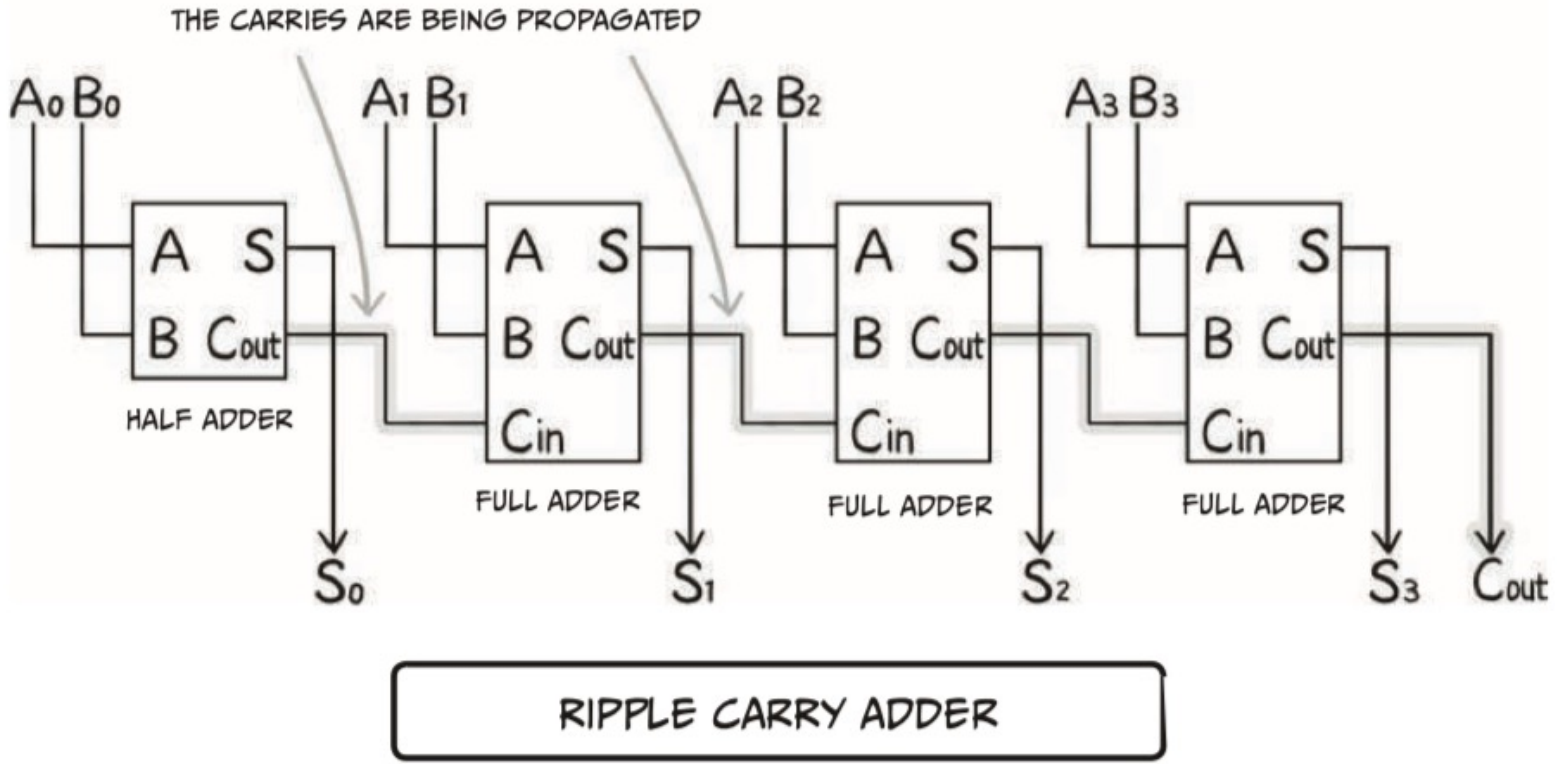


Adder

The 8-Bit Adder Principle

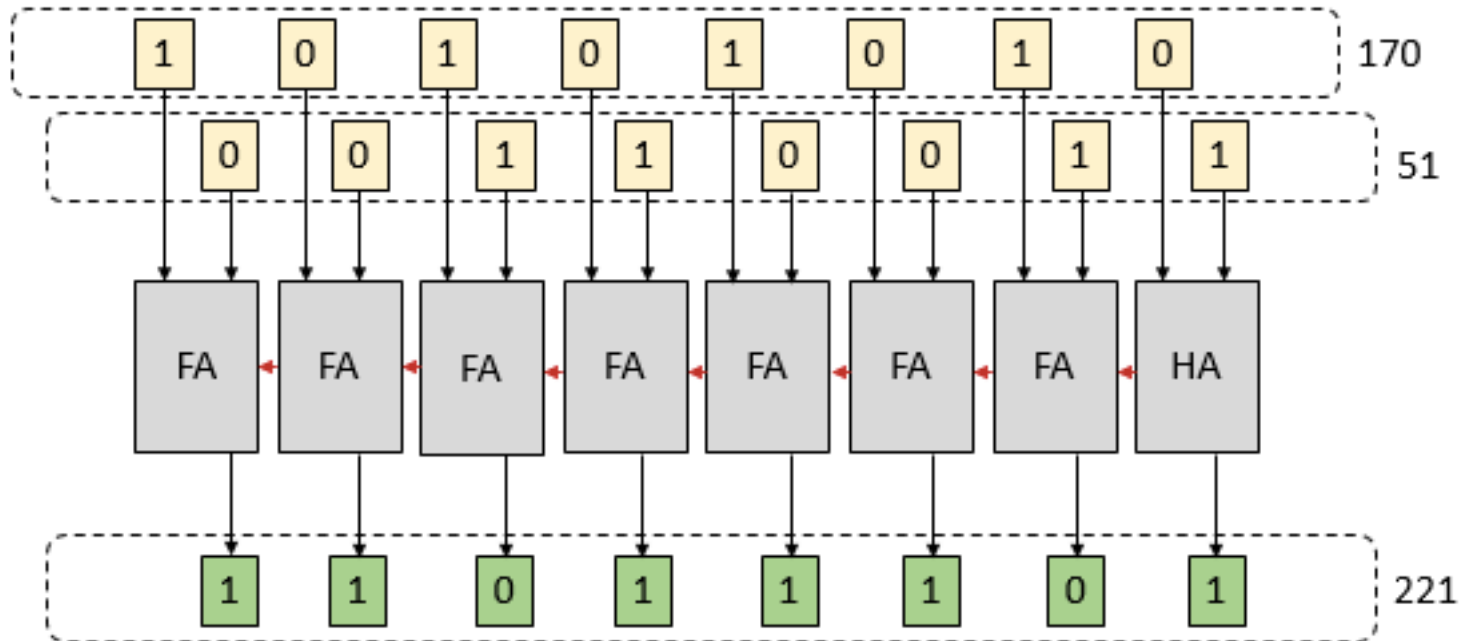The 8-bit adder adds the numbers digit by digit, as can be seen in the schematic diagram below. In this example, the integers 170 and 51 represent input a and b, respectively, and the resulting output is the sum 221. The first adder does not have any carry-in, and so it is represented by a half adder (HA) instead of a full adder (FA).



MIPS/MARS ALU

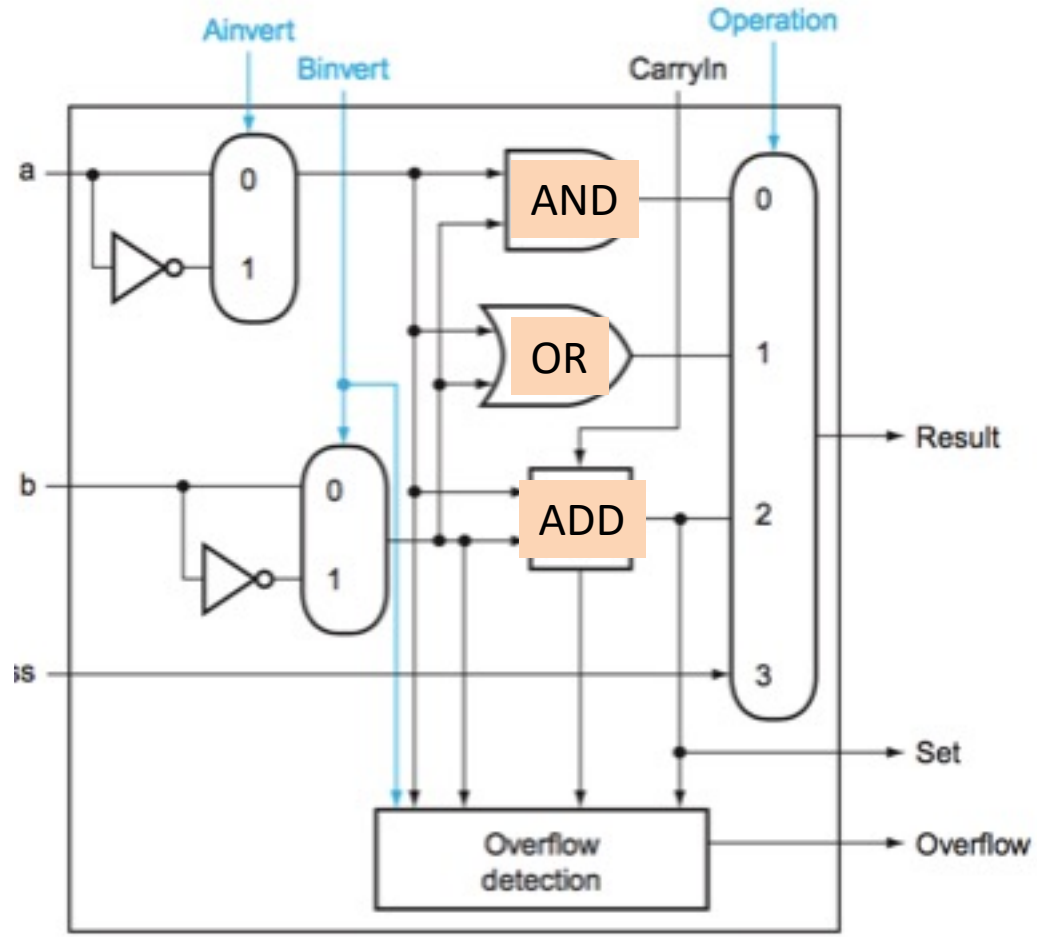

MIPS ALU in Verilog

HDL

Figure 8.5.15: A Verilog behavioral definition of a MIPS ALU (COD Figure B.5.15).

```
module MIPSALU (ALUctl, A, B, ALUOut, Zero);
    input [3:0] ALUctl;
    input [31:0] A,B;
    output reg [31:0] ALUOut;
    output Zero;

    assign Zero = (ALUOut==0); //Zero is true if ALUOut is 0
    always @(ALUctl, A, B) begin //reevaluate if these change
        case (ALUctl)
            0: ALUOut <= A & B;
            1: ALUOut <= A | B;
            2: ALUOut <= A + B;
            6: ALUOut <= A - B;
            7: ALUOut <= A < B ? 1 : 0;
            12: ALUOut <= ~(A | B); // result is nor
            default: ALUOut <= 0;
        endcase
    end
endmodule
```

AMD Products (1971)

- Analog
 - Op Amps
 - Voltage Regulators
- Packages
 - DIP
 - Others

Electronic Device Cos.

1972



(213) 870-7171

ORANGE COUNTY
(714) 522-8200
ZENITH 2-1474

STOCKING INVENTORY



IN EVERY LOCATION


Nationwide Distributor for the world's finest lines of quality electronic components!

HAMILTON ELECTRO SALES

10912 W. Washington Blvd. • Culver City, California 90230

- ADVANCED MICRO DEVICES** Integrated Circuits
- BOURNS** Potentiometers
- BURROUGHS** Nixie Tubes, Digital Displays
- FAIRCHILD** Semiconductors, Integrated Circuits,
Microwave & Opto Devices
- GENERAL ELECTRIC** Semiconductors, Capacitors,
Meters, Opto Devices, Relays,
Volt Pacs
- INTEL** Integrated Circuits
- KEMET** Solid Tantalum, Ceramic Capacitors
- LITRONIX** Opto Devices
- MEPCO/ELECTRA** Potentiometers, Resistors
- MONSANTO** Opto Devices
- MOTOROLA** Semiconductors, Integrated Circuits,
Opto Devices
- NATIONAL SEMICONDUCTOR** Semiconductors,
Integrated Circuits, Opto Devices
- POTTER & BRUMFIELD – WOOD** ... Relays, Switches,
Circuit Breakers
- RCA** Semiconductors, Integrated Circuits,
Opto Devices
- SIGNETICS** Integrated Circuits
- SILICONIX** Semiconductors, Integrated Circuits
- WESTINGHOUSE** Semiconductors

AMD Catalog 1971

 

AMD Analog (Linear)

LINEAR CIRCUITS

Operational Amplifiers

General-Purpose
 Frequency
 Compensated
 Dual
 747/747C
 (dual 741/741C)
 Single
 741/741C
 107/207/307

General-Purpose Frequency Compensated Operational Amplifiers

This class of circuit provides the trade-off of electrical parameters required for general-purpose linear and non-linear computing applications. These circuits should be input/output protected, latch-up free, Vos adjustable and pin-for-pin compatible with the 709.

General Purpose
 Uncompensated
 Dual
 Am1501
 (dual 101A)
 Single
 748/748C
 101A/201A/301A
 108/208/308
 101/201/301

General-Purpose Uncompensated Operational Amplifiers

Applications where amplifier phase margins will allow tailored-bandwidth operation in non-unity gain applications.

High-Speed Operational Amplifiers

The primary applications for these circuits are where interest


High Speed
 (10V/ μ sec)
 715/715C
 102/202/302
 110/210/310

Low Power
 108/208/308
 108A/208A/308A

Because of the high-performance of the application it may be of advantage for the amplifier to have bandwidth tailoring capability (not internally compensated). These applications do require competent understanding of gain phase and compensation the

Low-Power Operational Amplifiers

AMD Analog (Linear)

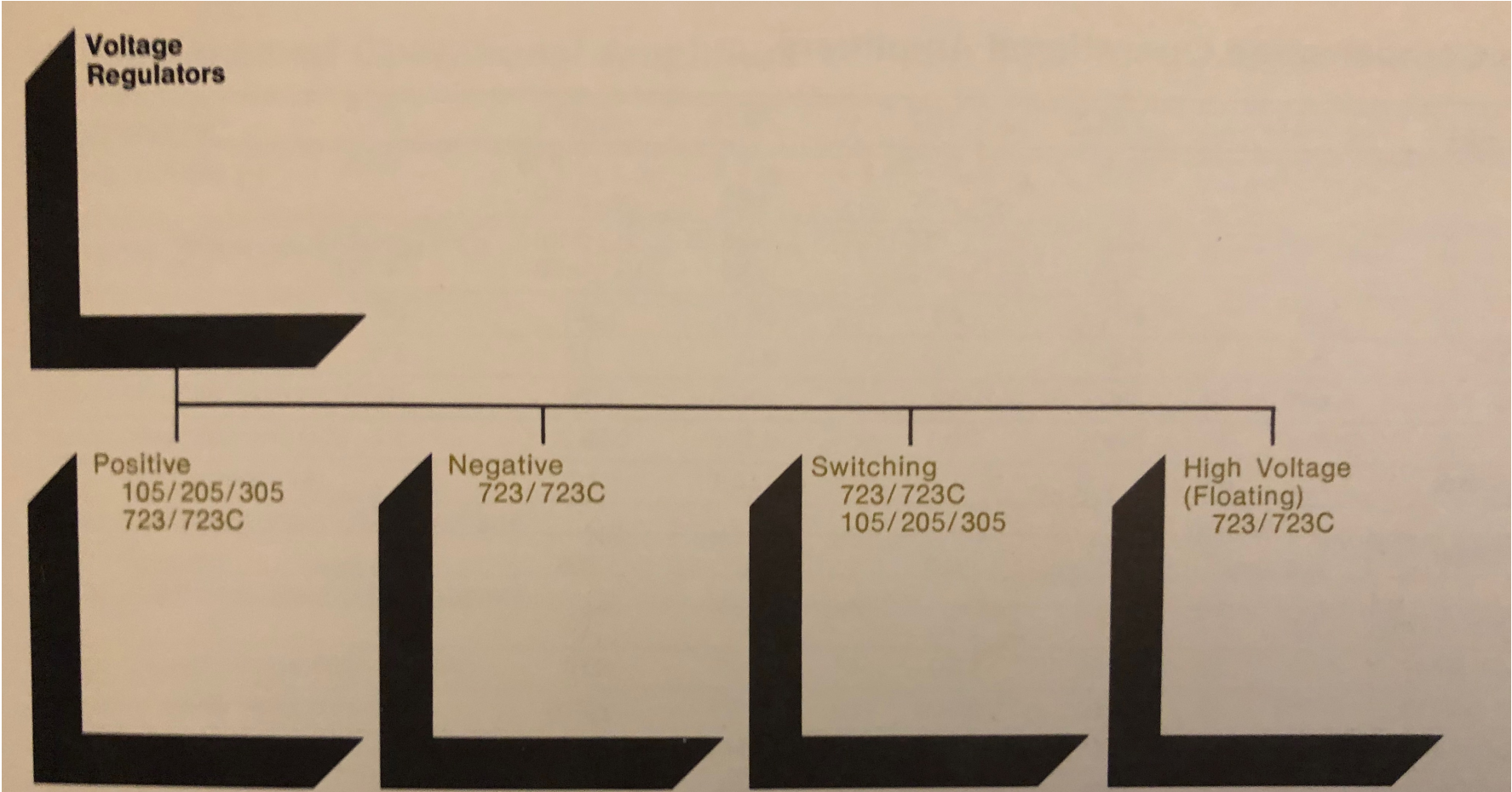






The monolithic regulator is considered useful for local-board regulation, amplifier supplies, and other applications where the size and economics are of advantage. Monolithic regulators should be considered in conjunction with exter-

nal-pass transistors when power out is important. Their primary advantage is ease of use and economic regulation for applications not requiring better than combined 1% line and load regulation over temperature.

Precision regulation is required when external reference devices are used.

AMD Packages

COMP122

     

Note: All dimensions are in inches.
 Leads are gold plated Kovar.

Logic

- Logic Product Lines
 - 54/7400
 - F9300/Am9300
- ALU slice (4-bit)
 - 54/74181
 - Am9340

AMD Digital MSI

1971

Am MSI Registers

Am9300 Four-Bit Shift Register
Am9328 Dual Eight-Bit Shift Register

Counters

Am2501 Binary Hexadecimal Up/Down Counter
Am8284 Binary Hexadecimal Up/Down counters
Am8285 BCD Decade Synchronous Up/Down Counter
Am9306 BCD Decade Synchronous Up/Down Counter
Am9310 BCD Decade Counter
Am9316 Four-Bit Binary Counter

Encoders

Am9318 Eight-Input Priority Encoder

Multiplexers

Am9309 Dual Four-Input Multiplexer
Am9312 Eight-Input Multiplexer
Am9322 Quad Two-Input Multiplexer

Latches

Am9308 Dual Four-Bit Latch
Am9314 Four-Bit Latch

Operators

Am54/74181 Four-Bit Arithmetic Logic Unit
Am54/74182 Look-Ahead Carry Generator
Am9304 Dual Full Adder
Am9324 Five-Bit Comparator
Am9340 Four-Bit Arithmetic Logic Unit
Am9341 Four-Bit Arithmetic Logic Unit
Am9342 Carry Look Ahead

Decoder and Demultiplexer

Am9301 Demultiplexer/One of Ten Decoder
Am9311 Demultiplexer/One of Sixteen Decoder

Logic IC's: ALU Slices

Bit-slice 1965-75

Texas Instruments


- ❖ Fairchild 9300 series
- ❖ Signetics
- ❖ National
- ❖ Motorola
- ❖ Texas Instruments

❖ **54/7400 Series**

- 54 → **Mil temp**
- 74 → **Com'l temp**

❑ **54/74SN181**

➤ 4-bit **ALU slice**

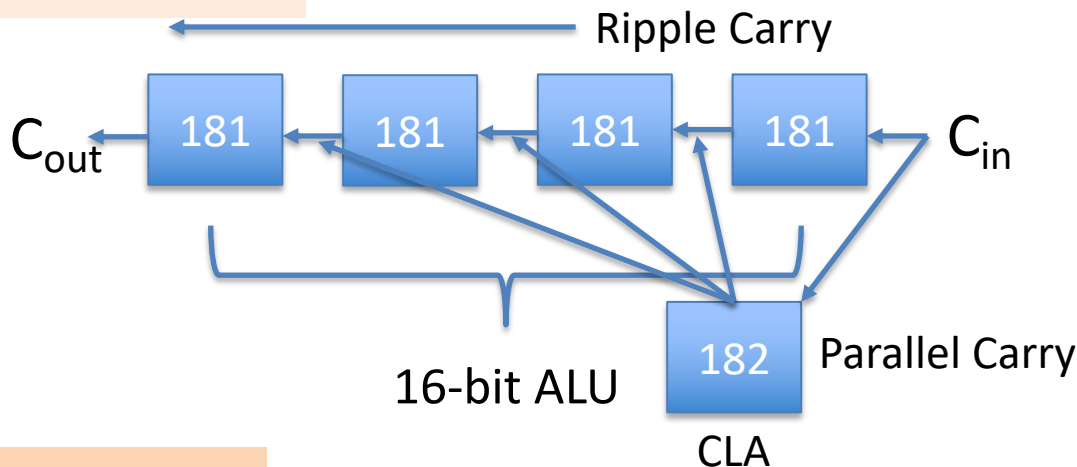

Am2505 2x4-bit
Multiplier slice

➤ 4-bit **MPU slice**

Replaced by **Am2900 family** → Am2901

ALU + Register file *microprogrammed*

Am2910


Microprogram sequencer

Am2902

CLA

AMD ALU – Am9340


Logic Diagram/Symbols

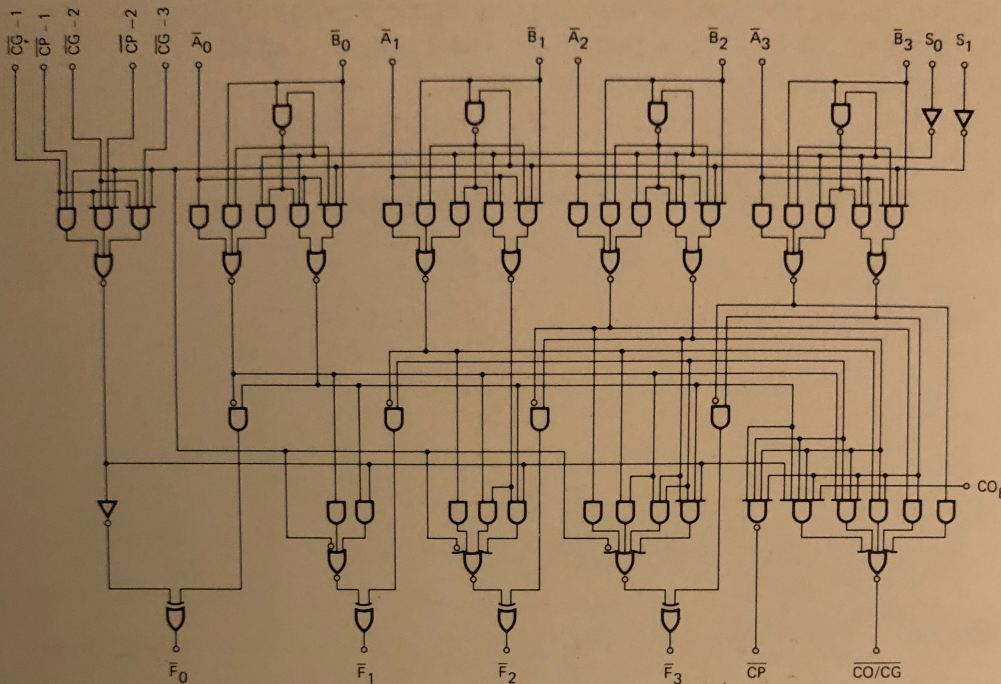


Characteristics

Typical Delays	Addition over 4 Bits	19 ns
	Addition over 16 Bits	33 ns
	Addition over 28 Bits	47 ns
Typical Power Dissipation		400 mW

Active LOW

 



Active HIGH

 

V_{CC} = Pin 24
GND = Pin 12

AMD CLA – Am9342

Logic Diagram/Symbol

 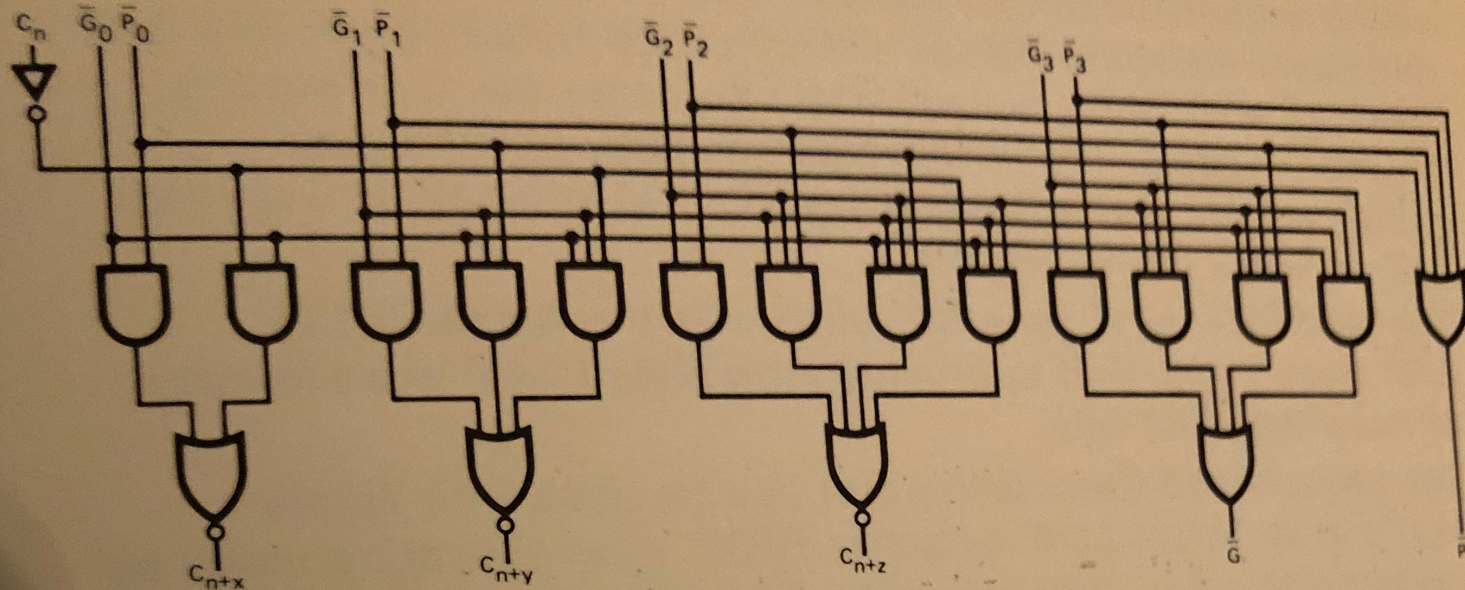

Characteristics

Typical Delay \bar{C}_{PO} to \bar{C}_P 7 ns
 C_{IN} to \bar{C}_P 13 ns
 Typical Power Dissipation 135 mW


V_{CC} = Pin 16
 GND = Pin 8

Section


Logic

- PIC
- Muxes
- Decoders
- Logic functions



PIC: Priority Interrupt Enc

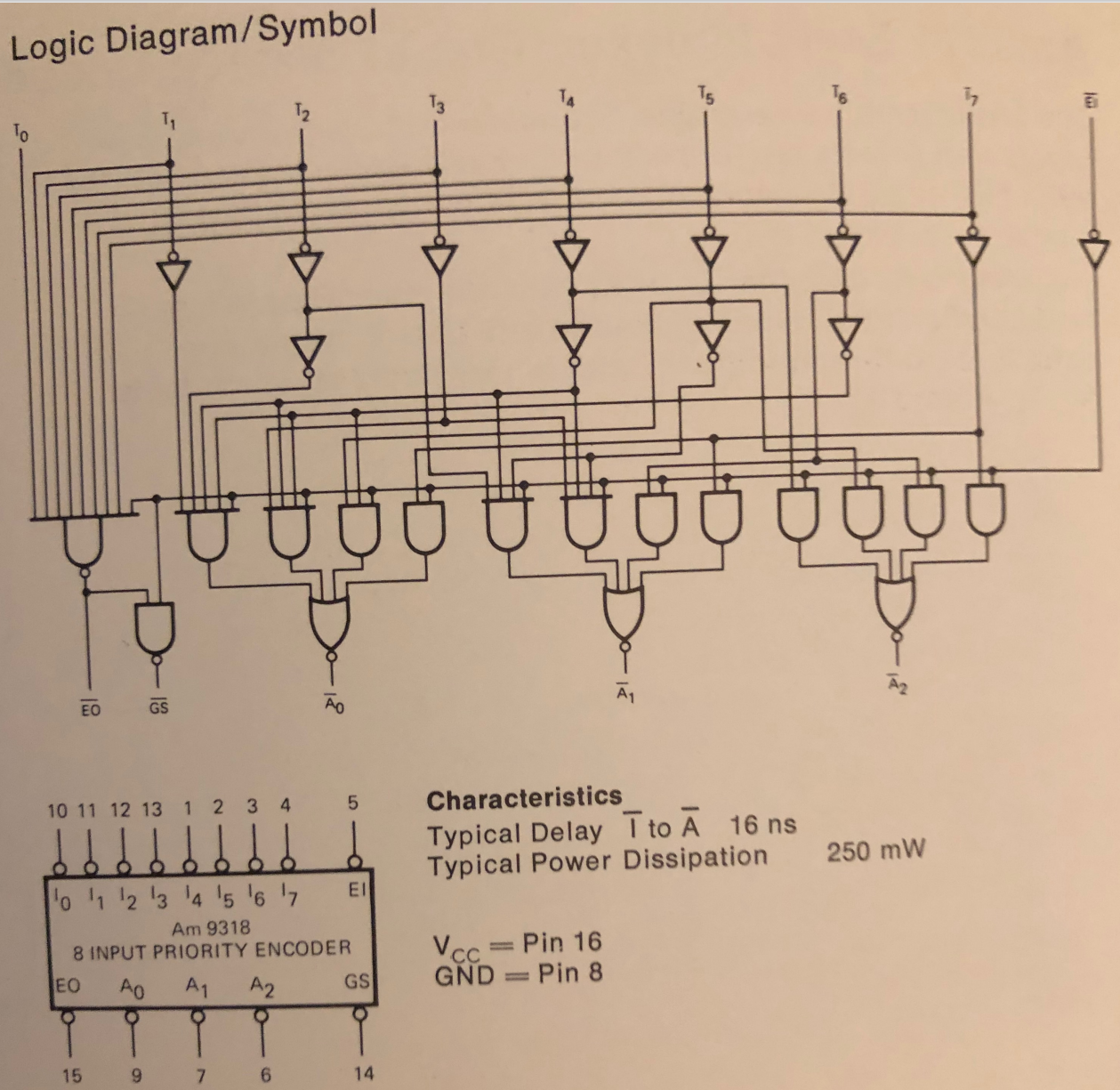


MUX

 

 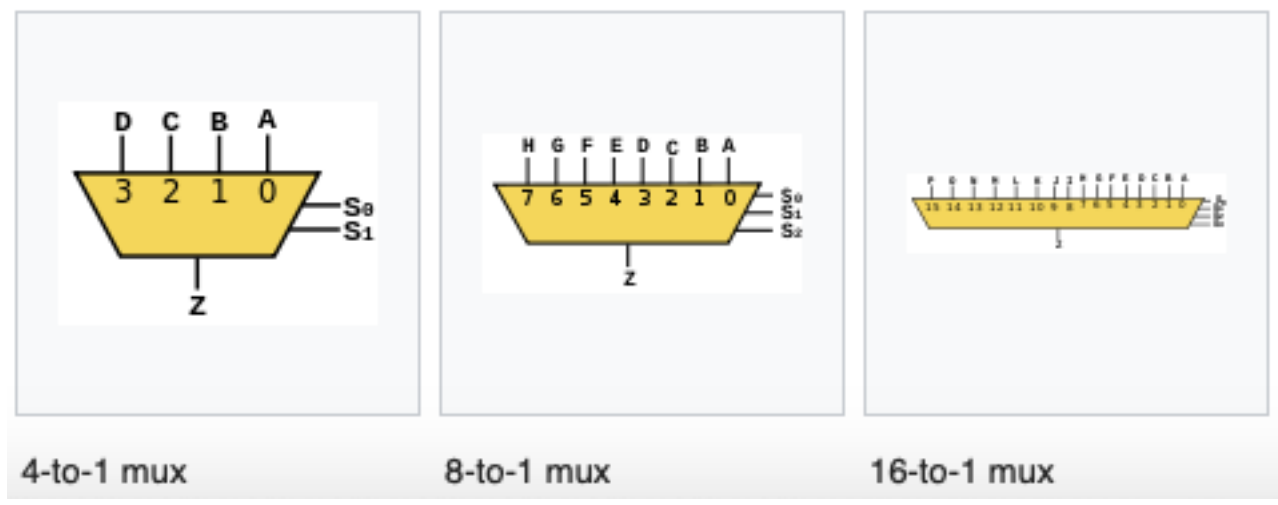The following 4-to-1 multiplexer is constructed from 3-state buffers and AND gates




MUX as Function Generator

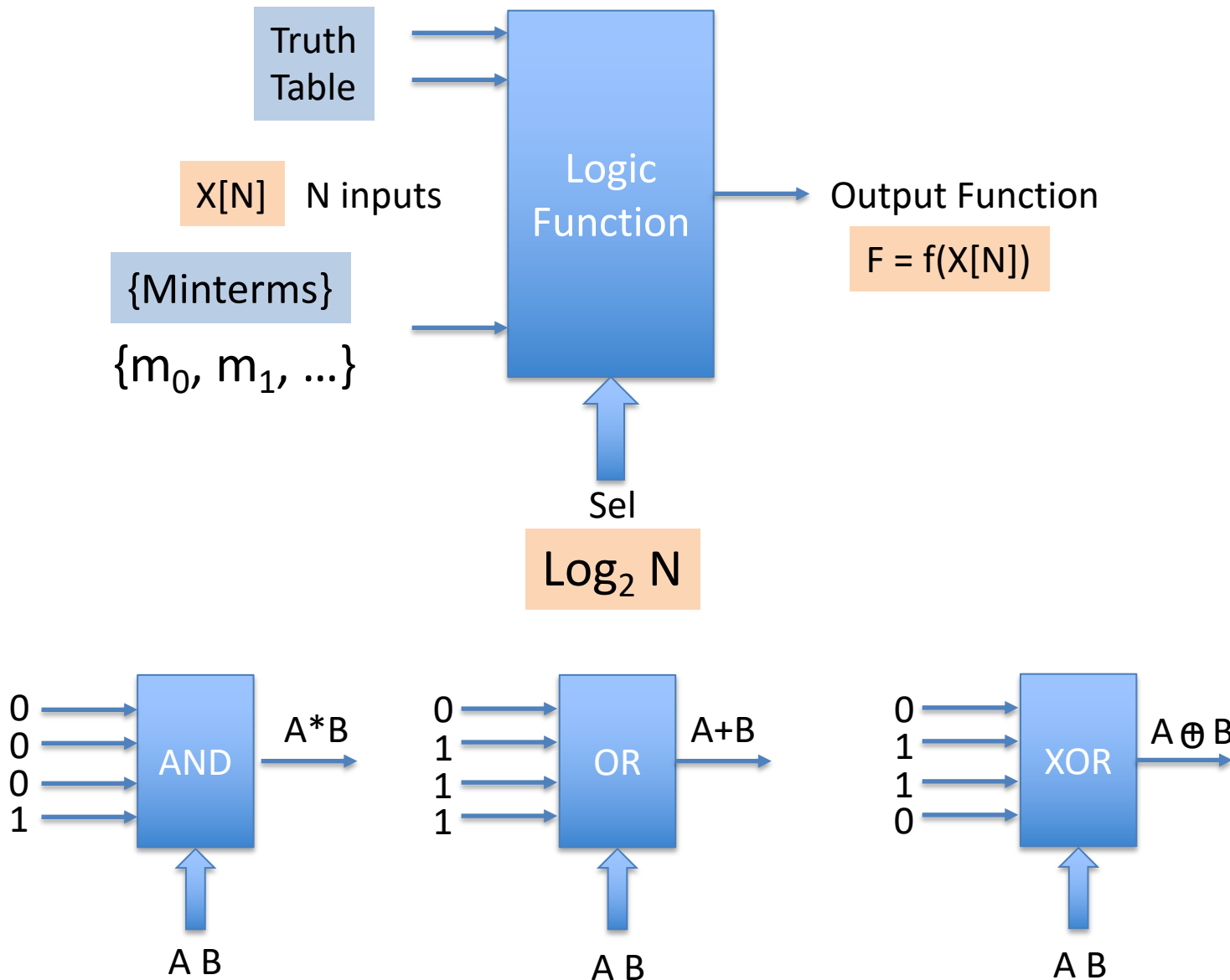

Full Adder via Mux

$$S = A \oplus B \oplus C_{in}$$

 


Mux Extension

{Minterms}


2x 2:1 mux \rightarrow 4:1 mux

$\{m_0, m_1, \dots\}$

 


AMD 8:1 Mux


Logic Diagram/Symbol

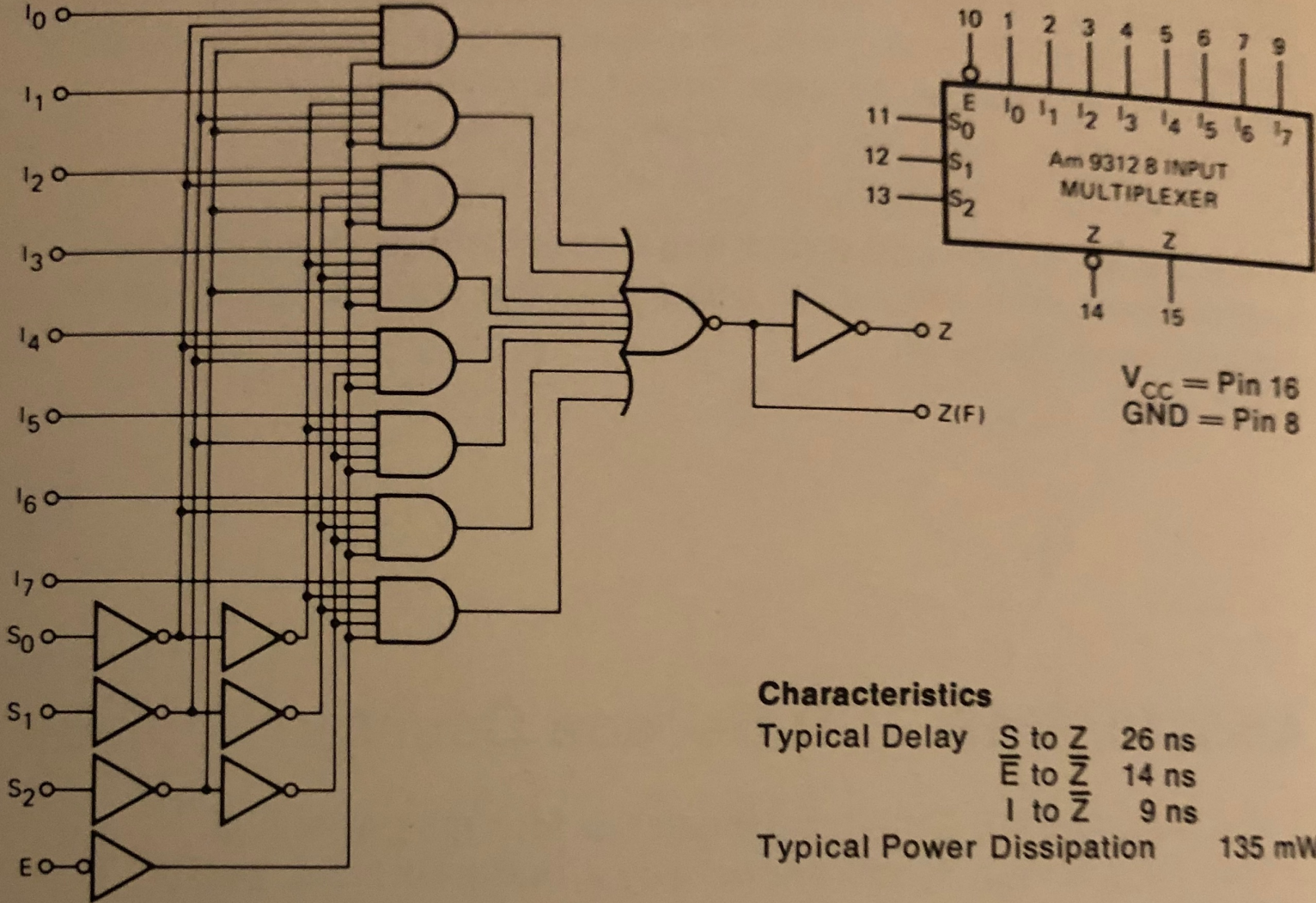

Decoder

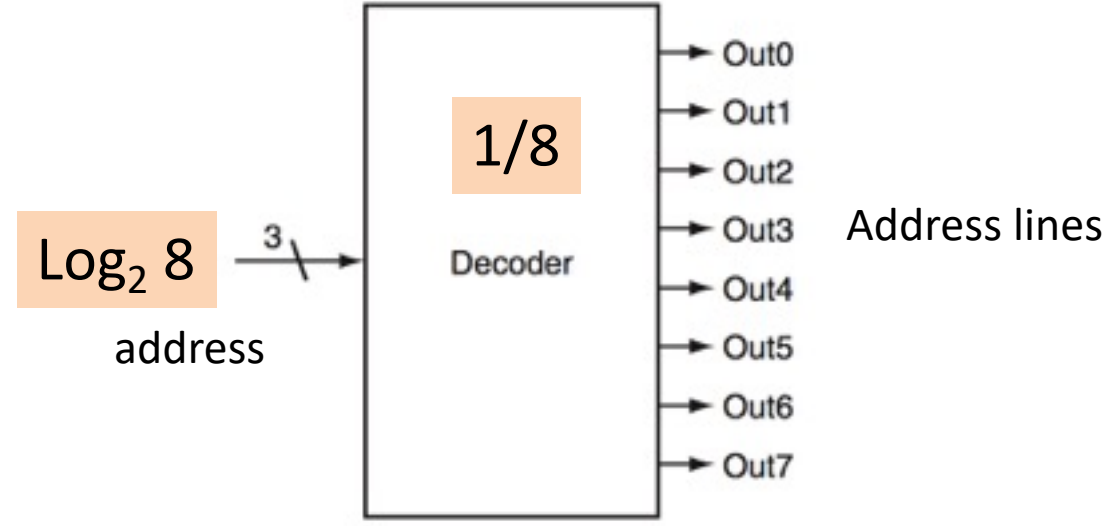

a. A 3-bit decoder

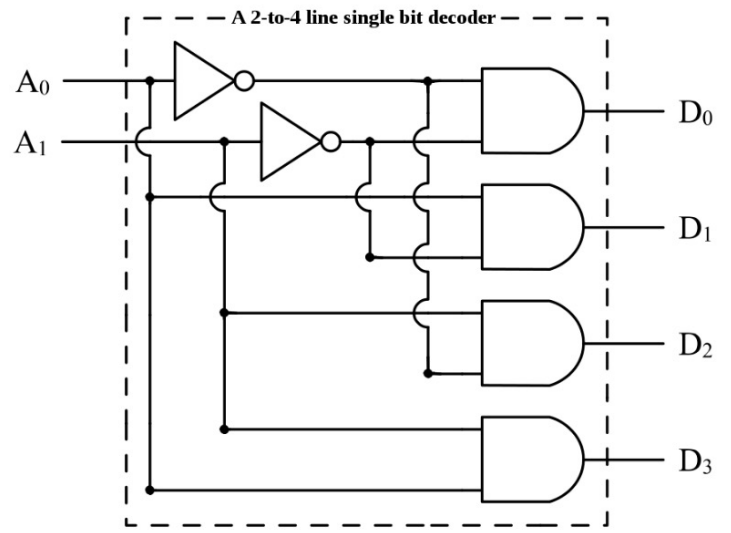

Truth Table

A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Minterm Equations

$$D_0 = \bar{A}_1 \cdot \bar{A}_0$$

$$D_1 = \bar{A}_1 \cdot A_0$$


$$D_2 = A_1 \cdot \bar{A}_0$$

$$D_3 = A_1 \cdot A_0$$

Decoder Expansion



DECODER EXPANSION

2x 2-to-4 \rightarrow 3-to-8 (1 of 8)

 

AMD Decoder (1/16)

Logic Diagram / Symbol

 
 


Characteristics
 Typical Delay A to Output 21 ns
 E to Output 17 ns
 Typical Power Dissipation 175 mW

V_{CC} = Pin 24
 GND = Pin 12

AMD Decoder (1/10)

Logic Diagram/Symbol

 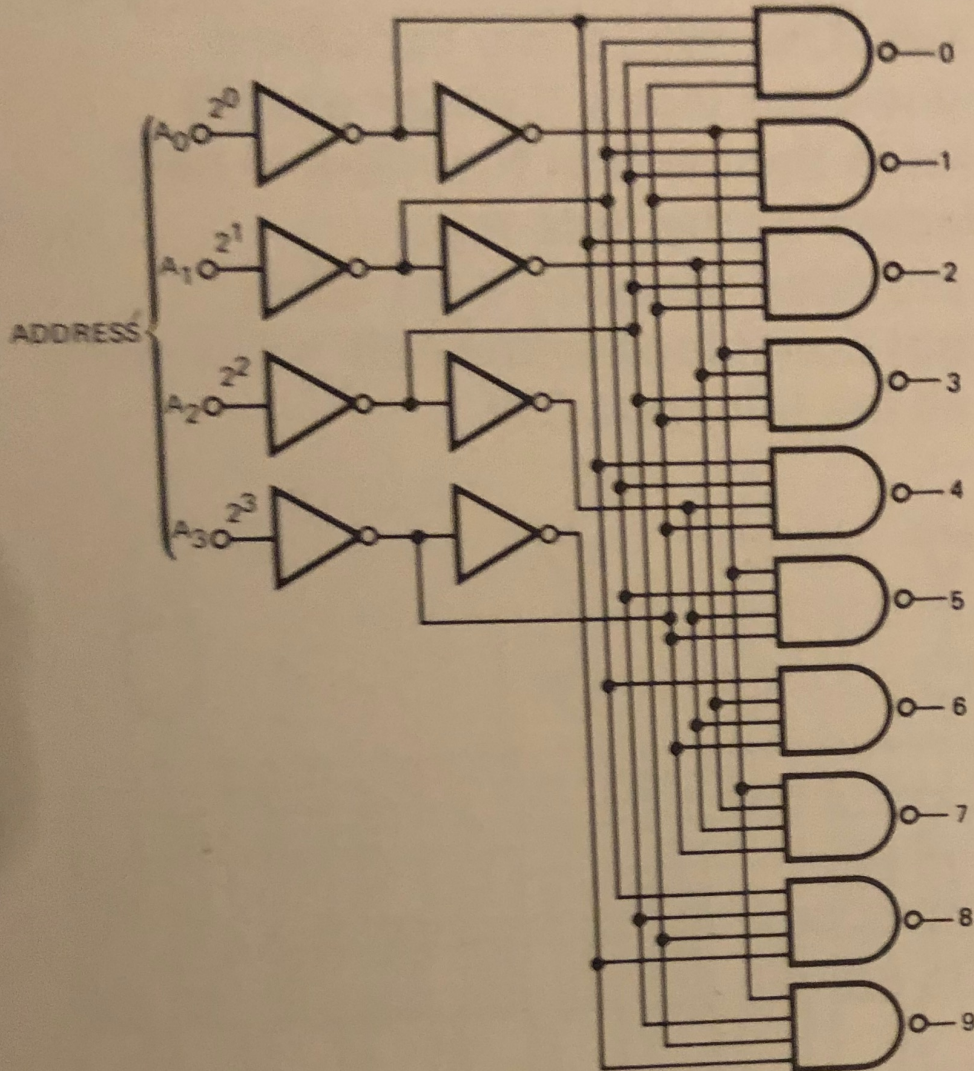


$V_{CC} = \text{Pin 16}$
 $GND = \text{Pin 8}$

Characteristics

Typical Delay A to Output 22ns
Typical Power Dissipation 145 mW


Register File Input Side

Decoders

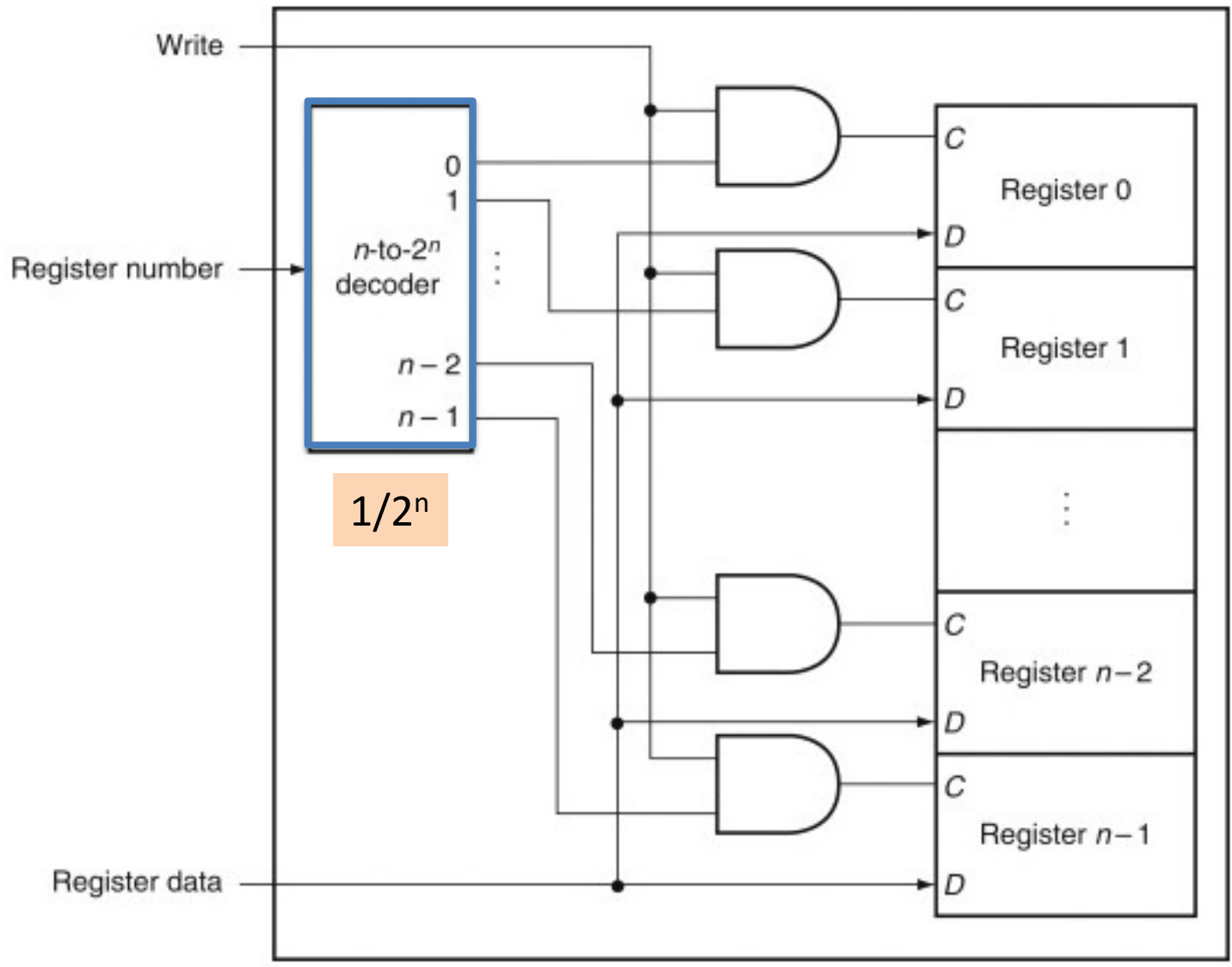


Register File on MARS

Decoders

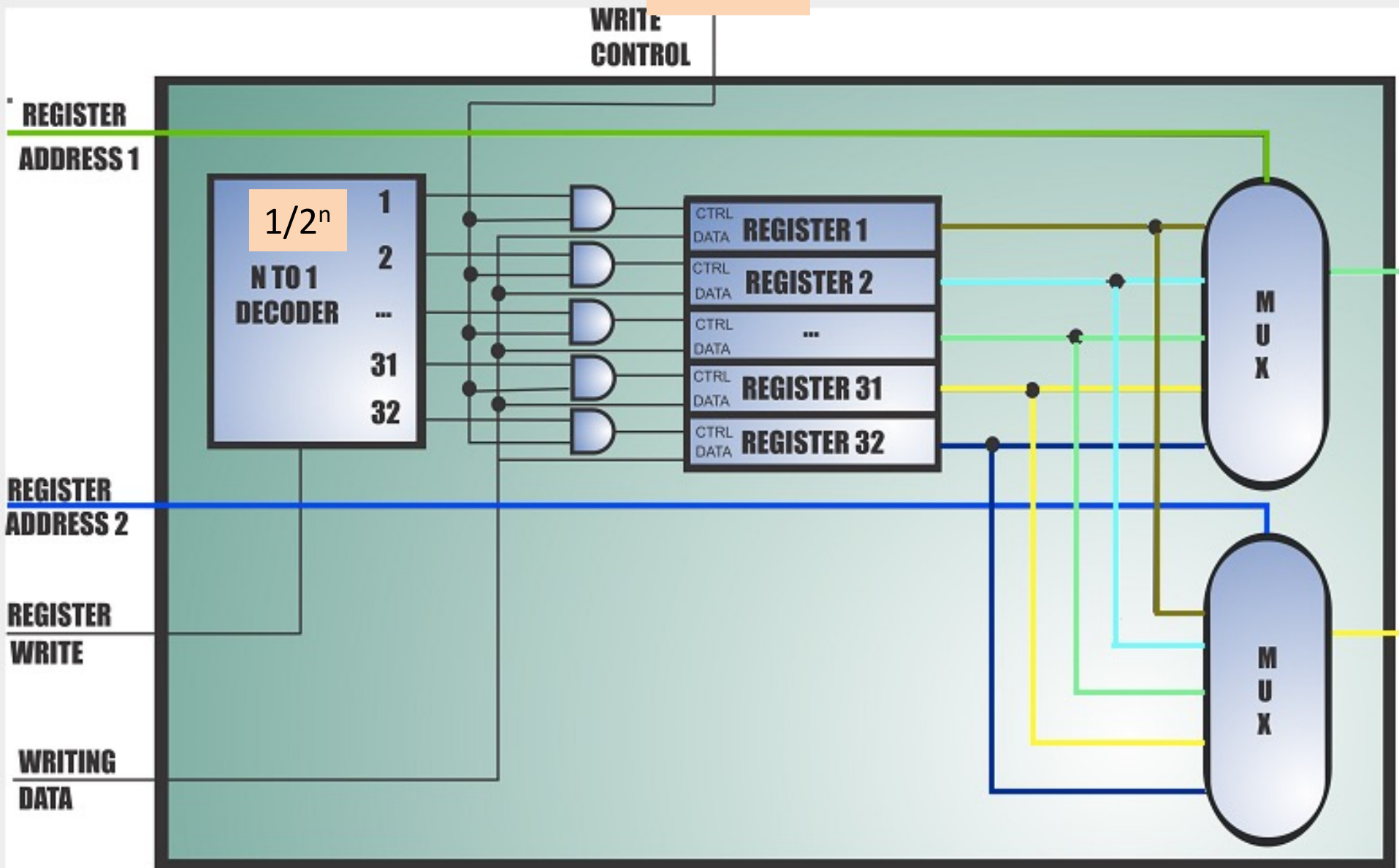

MIPS on MARS

REGISTER TYPE INSTRUCTION

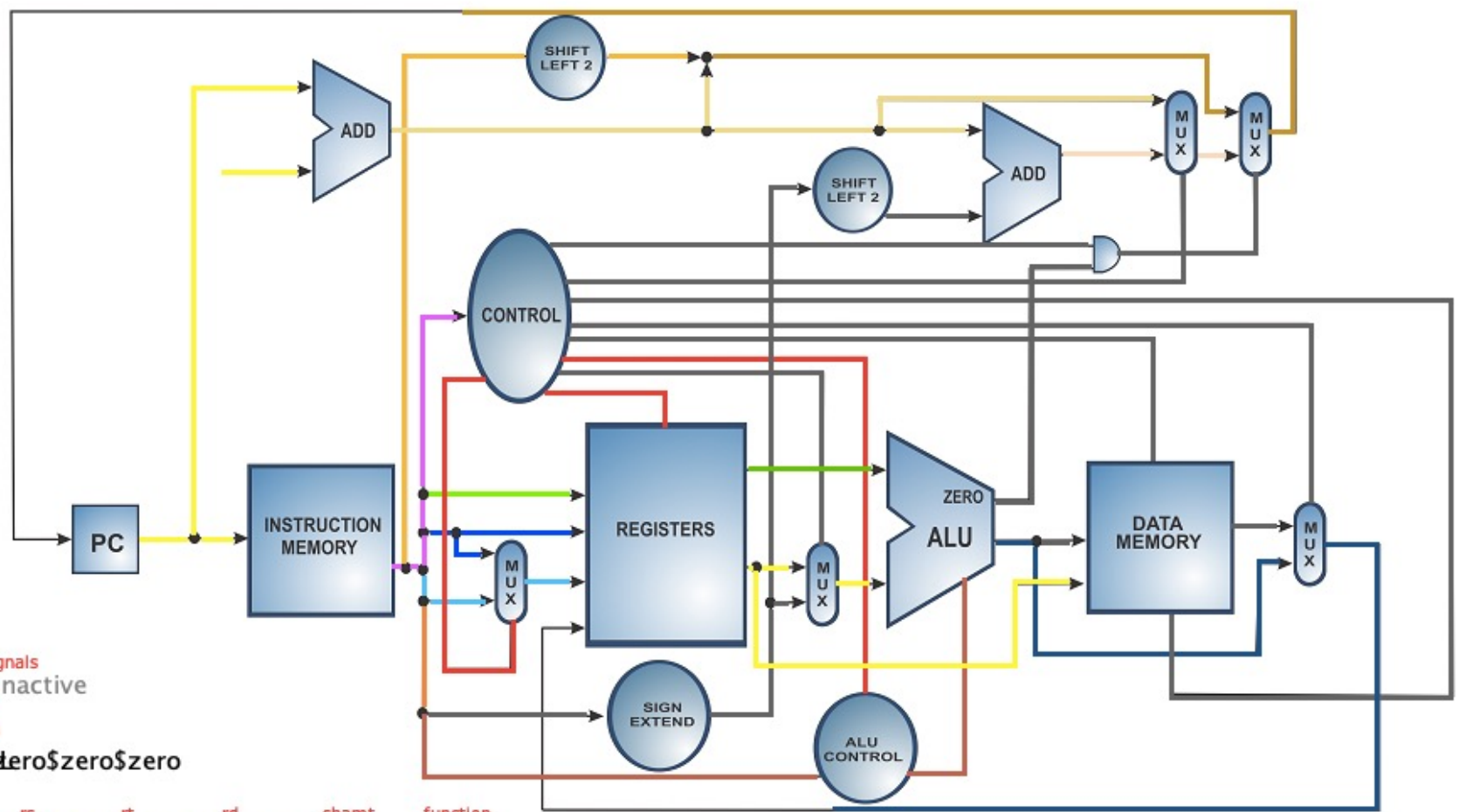

Control Signals
 Active Inactive

Instruction
 SYSCALL zero\$zero\$zero

opcode	rs	rt	rd	shamt	function
000000	00000	00000	00000	00000	001100

To see details of control units and register bank click inside the functional block

Section



Logic Minimization



Encoder Example

COMP122

Quora

Related **How do I make a converter (from excess 3 code to 8-4-2-1bcd code) using only 2-to -1 MUX and not gate?**

The truth table for excess-3 code to binary code converter is given below. Being 0000, 0001, 0010 and 1101, 1110, 1111 as invalid excess-3 code, output is made don't care.

TRUTH TABLE

X_3	X_2	X_1	X_0	B_3	B_2	B_1	B_0
0	0	0	0	x	x	x	x
0	0	0	1	x	x	x	x
0	0	1	0	x	x	x	x
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	0	1	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

$$B_0 = \{m_4, m_6, m_8, m_{10}, m_{12}\}$$

$$B_1 = \{m_5, m_6, m_9, m_{10}\}$$

$$B_2 = \{m_7, m_8, m_9, m_{10}\}$$

$$B_3 = \{m_{11}, m_{12}\}$$

INVALID
Excess-3
Code

INVALID
Excess-3
code

Logic Function Minimization

Combinational


❖ Quine-McKluskey

- ❑ Prime implicants
- ❑ Essential PI's

❖ Karnaugh ("K") Maps

Sum of Products: *minterms*

 
General form $F(x, y) = \{m_0, m_1, m_2, m_3\}$



Example $F(x, y) = \{m_0, m_1\} = x'y' + xy' \rightarrow y'$

K-Maps

Example

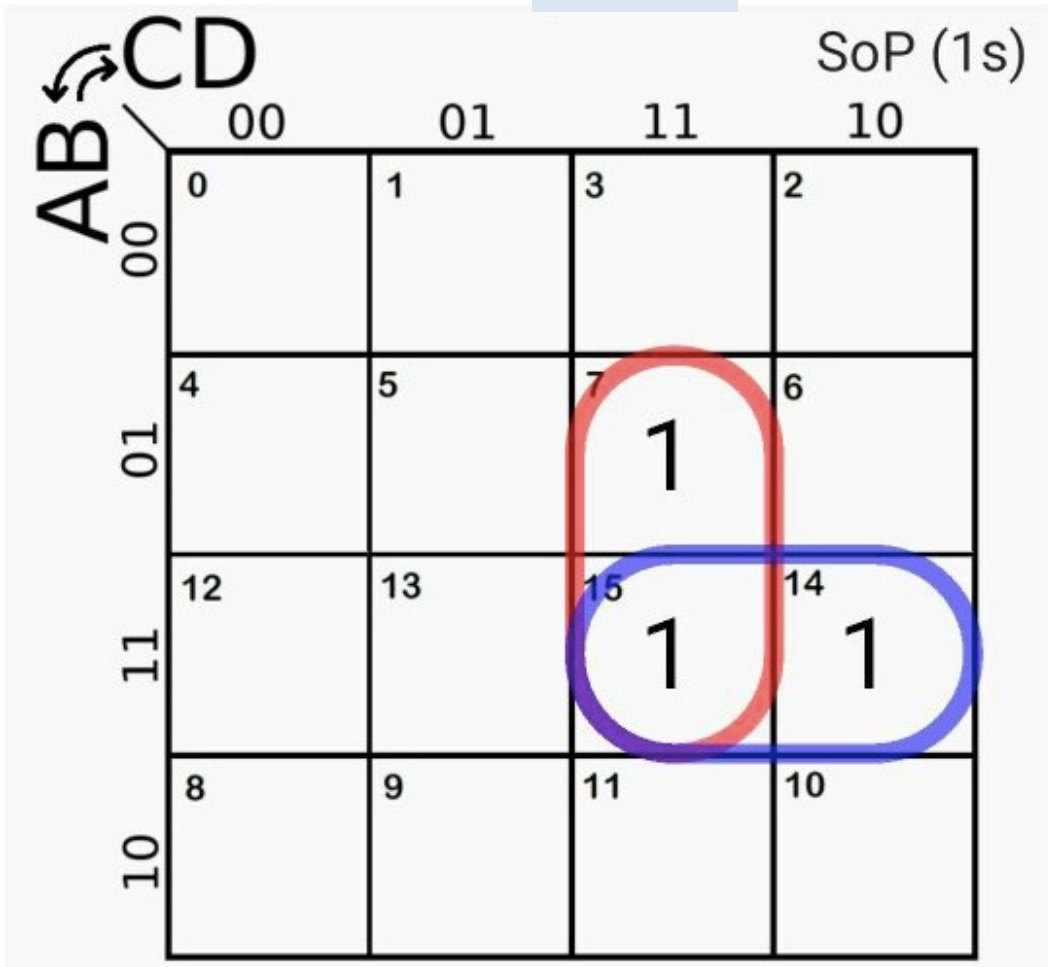

Gray codes

Logic distance=1

Select answer #1 / 1


$$S = BCD + ABC$$

K-Maps

Quora

Example

CD

 

Gray codes


Logic distance=1

$$S = \bar{D}$$

K-Maps

Quora

Example

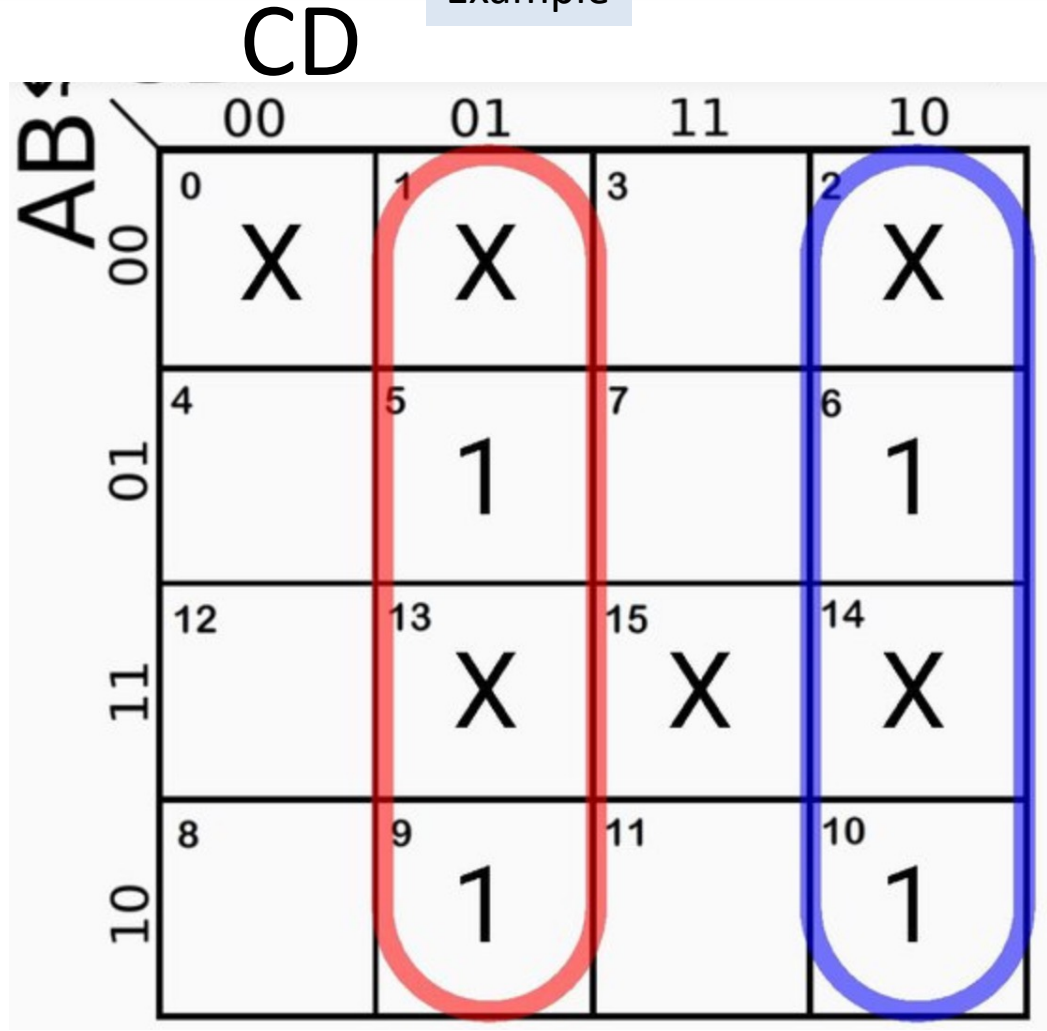

Gray codes

Logic distance=1


$$S = \bar{C}D + C\bar{D}$$

K-Maps

Quora

Example

CD

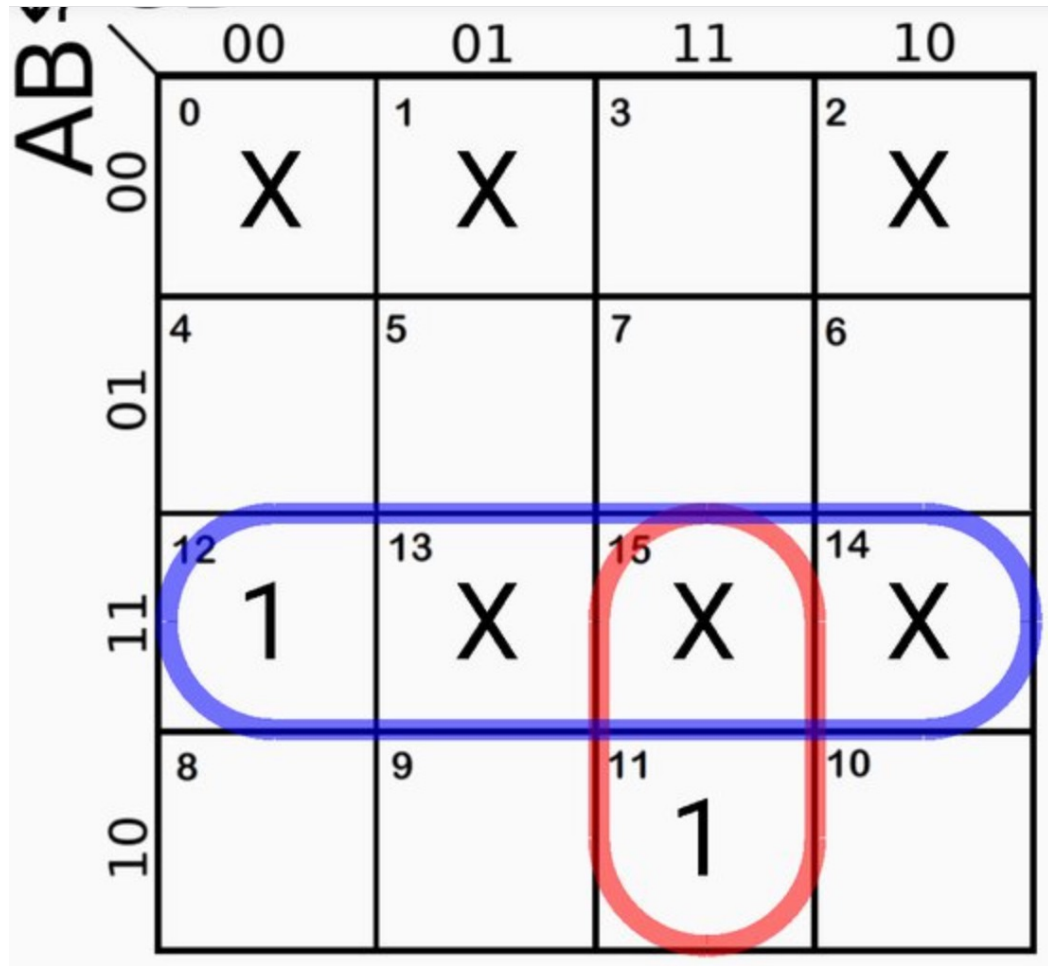

Gray codes

Logic distance=1


$$S = ACD + AB$$



K-Maps

Quora

Example

 

Gray codes

Logic distance=1

$$S = BCD + \bar{B}\bar{C} + \bar{B}\bar{D}$$

Section

Memory



- SRAM
- DRAM

AMD 64-Bit Bipolar SRAM

Am3101

1971

Logic Diagram/Symbol

 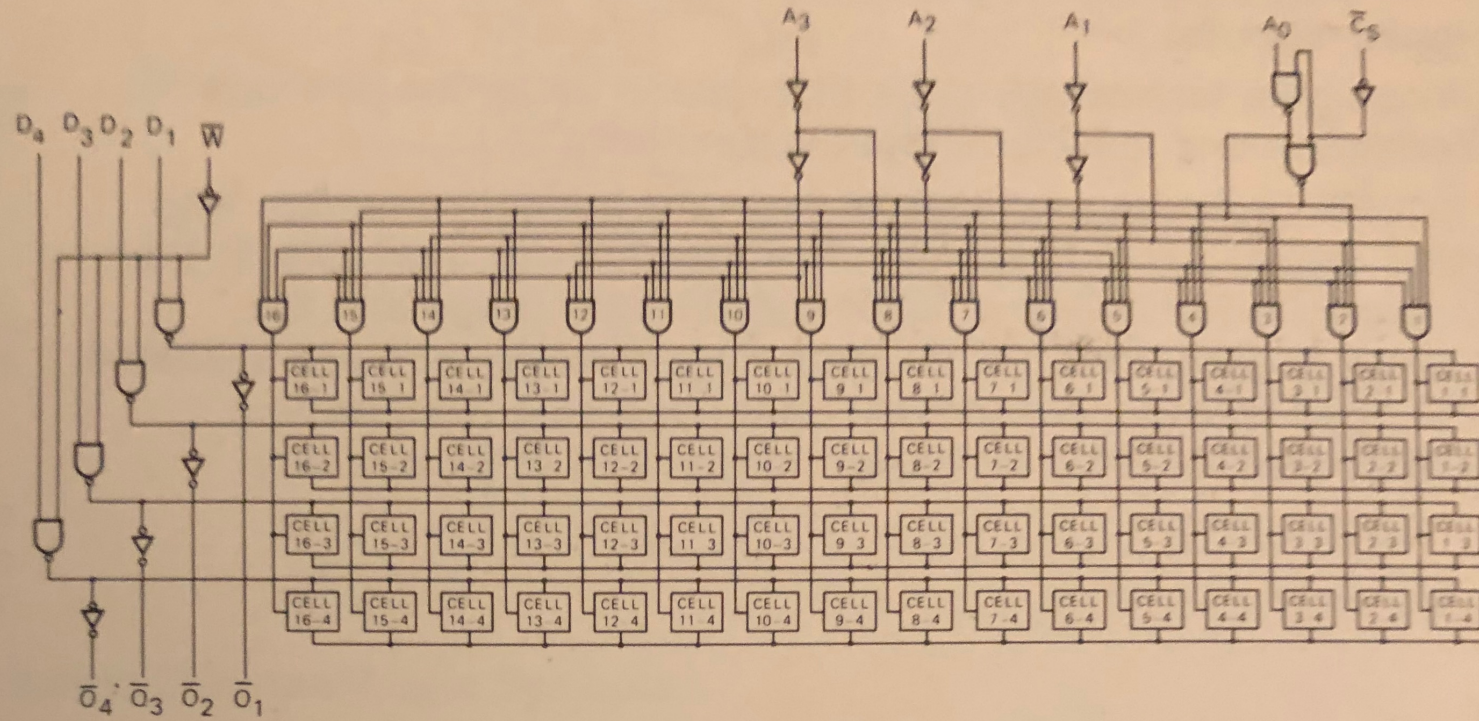

Characteristics 3101

Typical Delay Access Time 35 ns
 Typical Power Dissipation 400 mW

V_{CC} = Pin 16
 GND = Pin 8

AMD MOS LSI

1971

MOS/LSI

MOS is a technology of today as well as tomorrow. Various MOS technologies have been developed, but we feel silicon gate to be the most promising. Silicon gate will be the primary technology used for memory – application MOS products from Advanced Micro Devices. The basis for this decision is:

1. It is directly TTL and DTL compatible
2. It has greater speed than conventional metal-gate MOS
3. It is more reliable
4. Its reproducibility is higher
5. It is lower cost on a per-function basis


Our commitment in MOS is to produce large-chip standard circuits. The circuits are to have a broad customer base, and be available in full military temperature range (-55°C to $+125^{\circ}\text{C}$) as well as the commercial temperature range (0°C to $+75^{\circ}\text{C}$). Future plans call for the following additions to our product line in 1971:

256-Bit Static Random Access Memory

1024-Bit Dynamic Two-Phase Shift Register
(1024x1, 512x2, 256x4)

1024-Bit Dynamic Random Access Memory


Am1101A 256x1 SRAM

 

DRAM (AMD 1Kx1)

Am1103A

1971

 


Logic

- Sequential
 - Flip-flops
 - Latches
 - Counters

Sequential Logic: Flip-Flops

Clocked

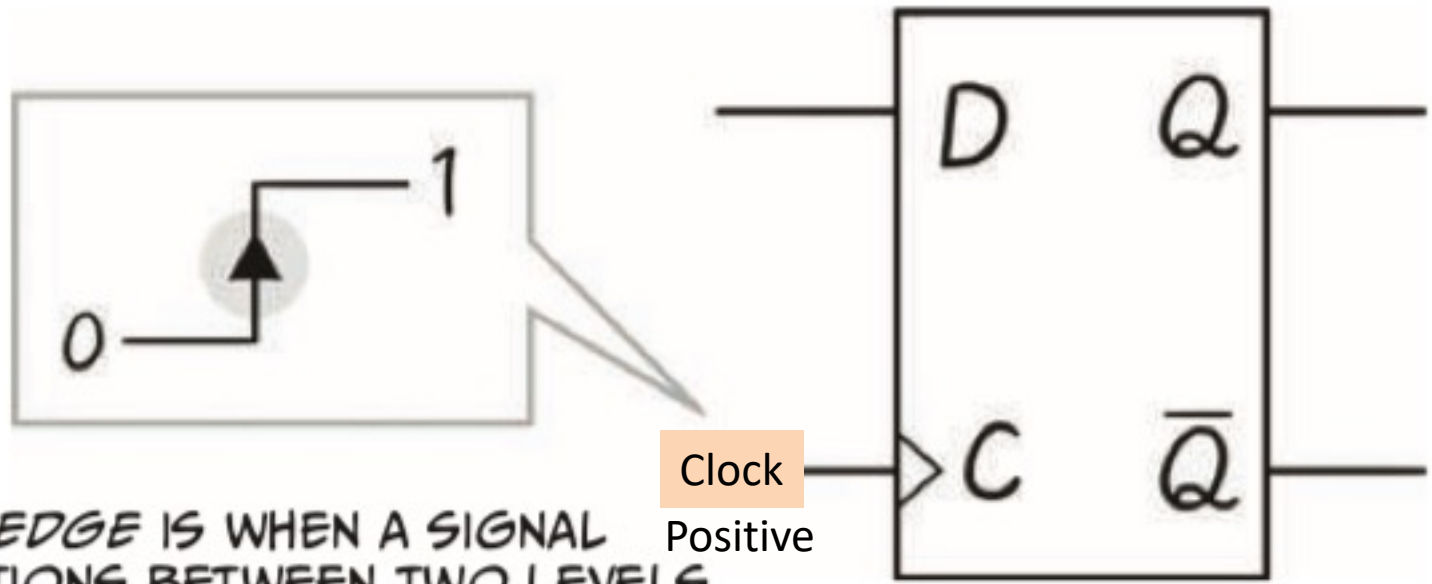


AN EDGE IS WHEN A SIGNAL
TRANSITIONS BETWEEN TWO LEVELS
(0 AND 1 FOR EXAMPLE).

Sequential Logic: Flip-Flops


[from Wikipedia]

Clock	D	Q _{next}
Rising edge	0	0
Rising edge	1	1
Non-Rising	X	Q

 


D flip-flop symbol

"D" FF

 


 A master-slave D flip-flop. It responds on the falling edge of the enable input (usually a clock)




An implementation of a master-slave D flip-flop that is triggered on the rising edge of the clock

Timing: setup, hold, delay

 


Flip-flop setup, hold and clock-to-output timing parameters


Other FFs

 

A circuit symbol for a T-type flip-flop

 


 A circuit symbol for a positive-edge-triggered JK flip-flop




A JK flip-flop made of NAND gates

Sequential Logic: SR Latch

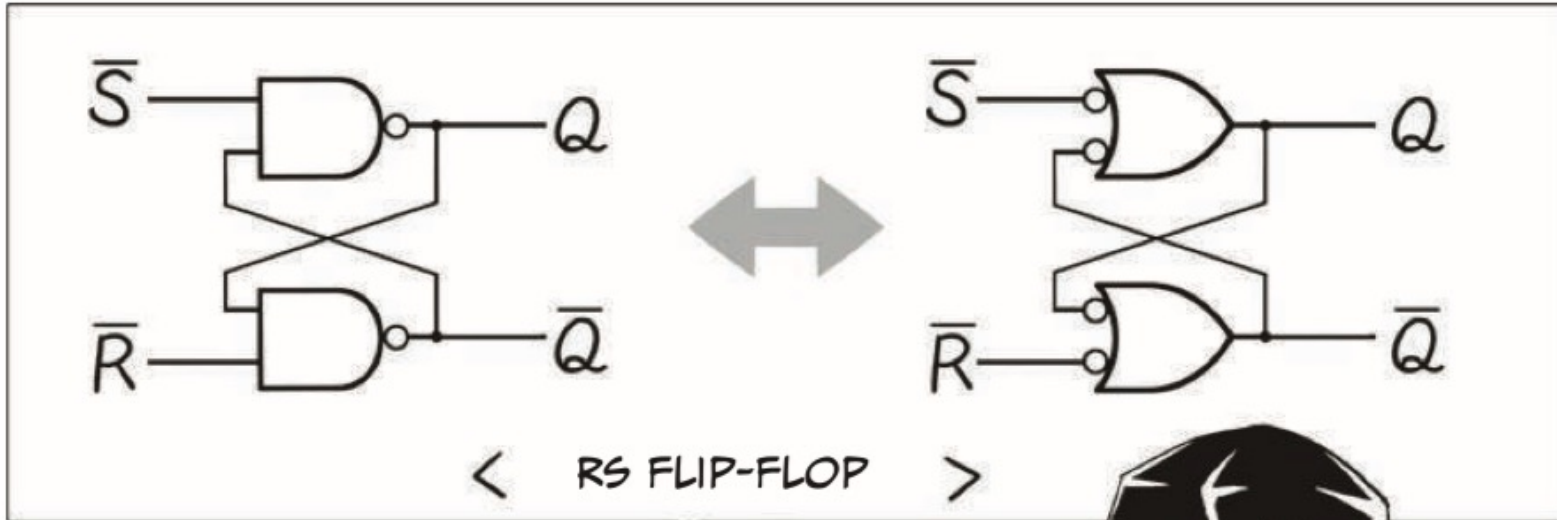




INPUTS		OUTPUTS		FUNCTION
\bar{S}	\bar{R}	Q	\bar{Q}	
1	1	DOES NOT CHANGE		RETAINS ITS CURRENT OUTPUT
0	1	1	0	SET
1	0	0	1	RESET
0	0	1	1	NOT ALLOWED

 

Sequential Logic: Latches

$\overline{S}\overline{R}$ latch operation




\overline{S}	\overline{R}	Action
0	0	not allowed
0	1	$Q = 1$
1	0	$Q = 0$
1	1	No Change

   

[from Wikipedia]

Gated D latch truth table



E/C	D	Q	\overline{Q}	Comment
0	X	Q_{prev}	\overline{Q}_{prev}	No change
1	0	0	1	Reset
1	1	1	0	Set

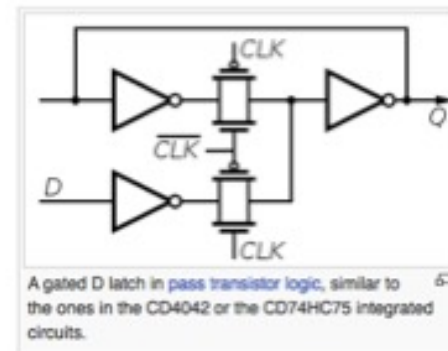  


Clocking




When the clock goes from low to high (0 to 1), we see a rising edge, and when it goes back from high to low (1 to 0), we see a falling edge.

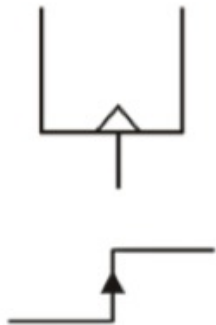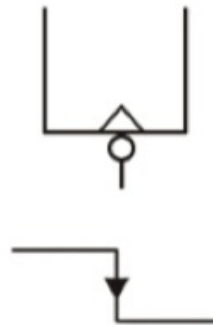RISING EDGE	FALLING EDGE
	
WHEN THE CLOCK GOES FROM LOW TO HIGH	WHEN THE CLOCK GOES FROM HIGH TO LOW

T: Toggle Flip-flop

 

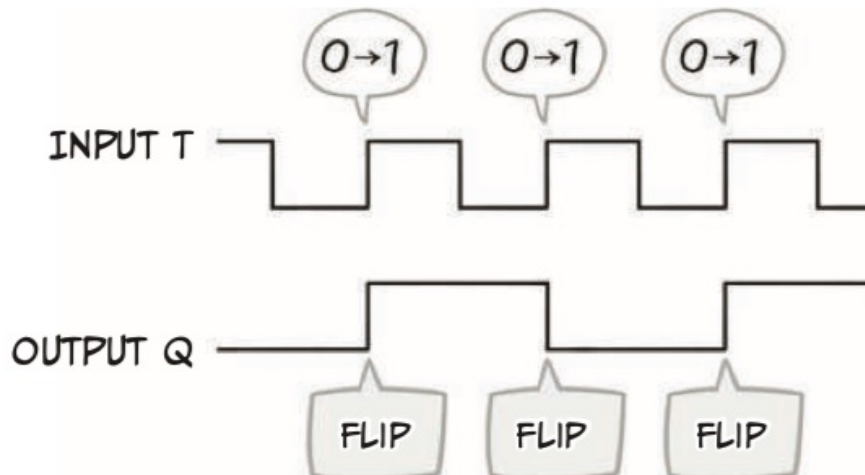Fuhahaha! Like I would ever forget! The *T flip-flop* only has one input, as you can see, and is pretty simple. Whenever the input *T* changes from 0 to 1, or 1 to 0, the output stored in *Q* flips state. It looks something like this time chart.




THERE ARE T
FLIP-FLOPS THAT
ACTIVATE JUST ON
FALLING EDGES
INSTEAD (1 TO 0).

Counter


Toggle

 By the way, flipping between 1 and 0 is called *toggling* . The *T* in T flip-flop actually stands for *toggle* ! Also, by connecting several T flip-flops together as in the schematic below, you can make a circuit that can count—a counter circuit.




THIS CIRCUIT SHOWS HOW SEVERAL T FLIP-FLOPS TOGGLED BY THE FALLING EDGE OF AN INPUT SIGNAL CAN ACT AS A COUNTER.

COUNTER CIRCUITS

 


Falling edge triggered

Counter

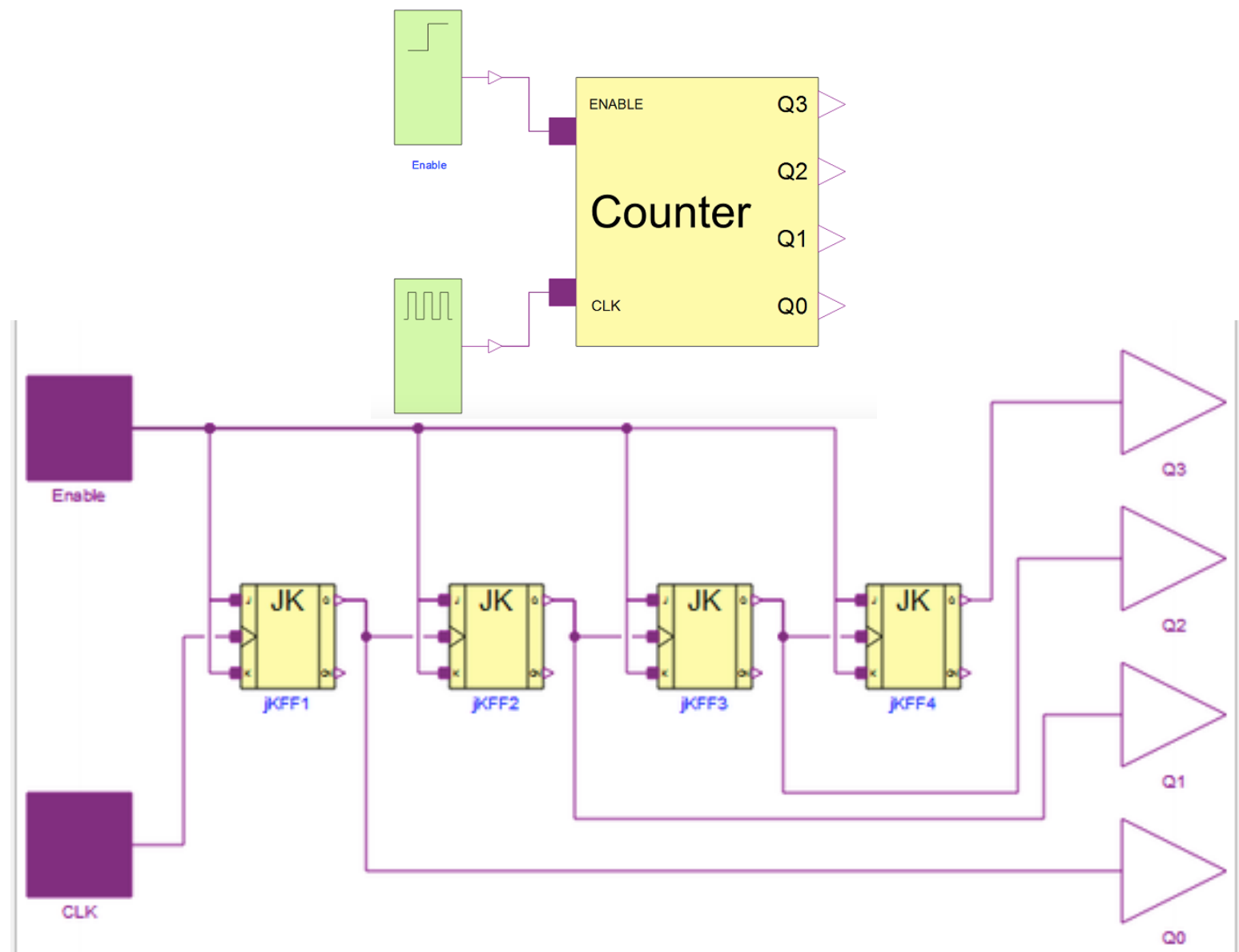


Counter

The counter in this example is a 4-bit asynchronous counter based on JK flip-flops. The flip-flops are connected with both their J and K terminals to the enable pin, putting them in "toggle mode". The flip-flop to the left, producing the Q0 signal, will change its output state for each falling edge of the clock signal, for example, a CPU clock. Since the output toggles for each falling edge of the clock, the clock toggles twice for each toggle of the output.

 

This diagram from a simulation shows how the logic levels of the four bits change over time. The enable signal goes from 0 to 1 after one second.

AMD Counter

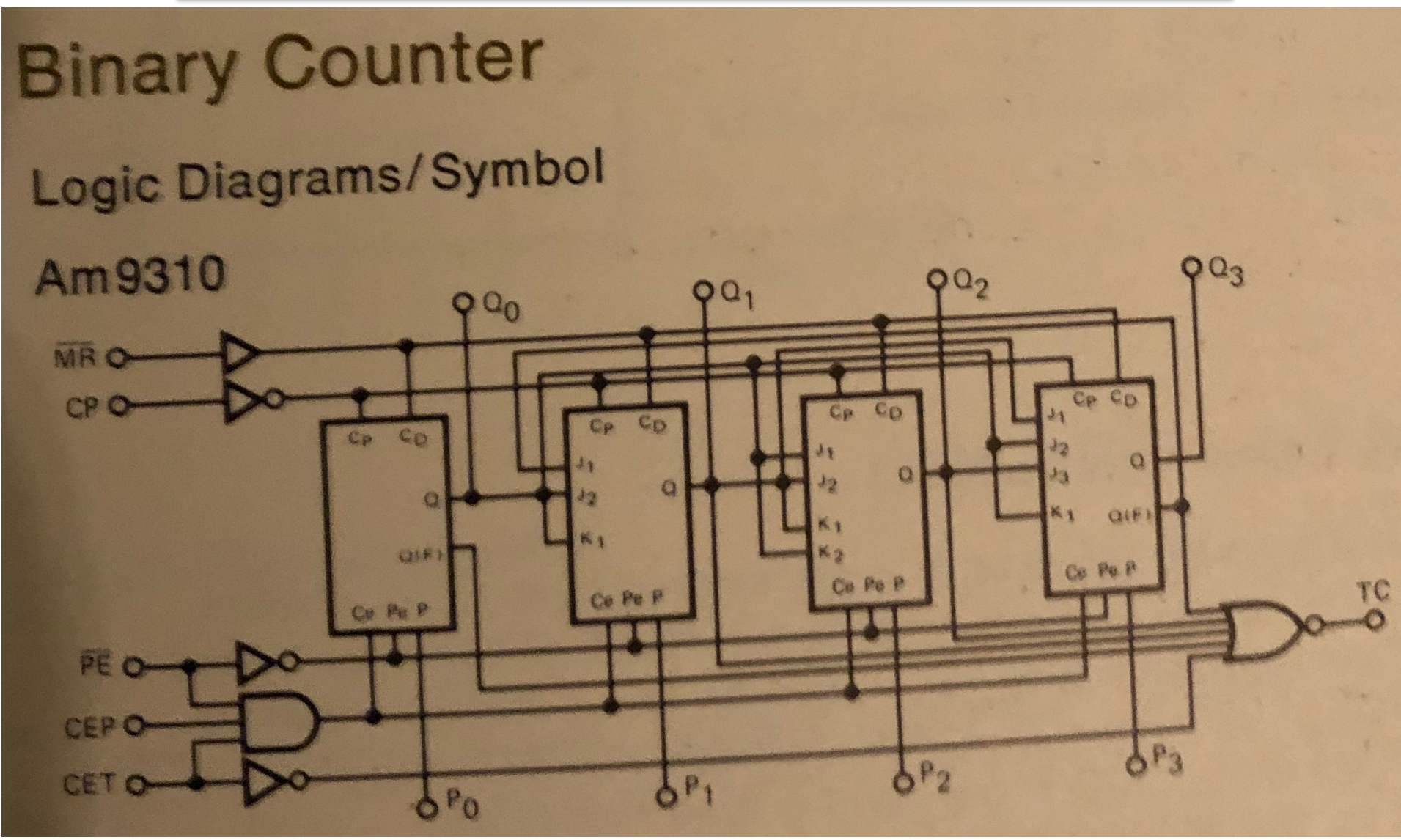

Section

Logic

- Multiplication
- Division

Binary Multiplication

Ancient Egyptian multiplication

From Wikipedia, the free encyclopedia
(Redirected from [Russian peasant algorithm](#))

In [mathematics](#), **ancient Egyptian multiplication** (also known as **Egyptian multiplication**, **Ethiopian multiplication**, **Russian multiplication**, or **peasant multiplication**), one of two multiplication methods used by scribes, was a systematic method for multiplying two numbers that does not require the [multiplication table](#), only the ability to multiply and [divide by 2](#), and to [add](#). It decomposes one of the [multiplicands](#) (preferably the smaller) into a sum of [powers of two](#) and



Ancient *Peasant* Multiplication

Multiplication



Jeff Drobman · Just now

multiplication is usually done completely in hardware, via a 2D array of "XY(i) + C" multiplier modules, whereby each row generates a partial product of the next signed digit of the multiplier times the multiplicand. shifting occurs in the hardware placement of each row. this array can also be pipelined, so multiple operations can be performed in sequential concurrency.

(See the 1971 **Am2505** 2x4-bit multiplier slice, and my personal MS thesis.)

Binary Multiplication

Ancient *Peasant* Multiplication

How do I write an ARM (Assembly) program that determines the product of 2 numbers using Russian peasant multiplication?



Jeff Drobman · just now

Former Stock Trader and App Developer (2003–present)

first learn ARM assembly language. then, follow this algorithm:

1. determine the smaller operand (use a "compare" op) and make it the multiplier
2. create a table of 2x the larger operand (multiplicand)
3. sum the table entries where the binary bit position is 1, and skip the 0's.

Examples [\[edit \]](#)

This example uses peasant multiplication to multiply 11 by 3 to arrive at a result of 33.

13x238

Decimal:	Binary:	3x11	13	238	1101 (13)	11101110	(238)
11 3	1011 11		6	476	110 (6)	111011100	(476)
5 6	101 110		3	952	11 (3)	1110111000	(952)
2 12	10 1100		1	+1904	1 (1)	11101110000	(1904)
1 24	1 11000						
—	—						
33	100001			3094			

2's Complement Multiply

❖ Simple

- Convert *Multiplier* to positive if negative
- Invert *Multiplicand* (if needed)

❖ Booth's algorithm

- Use *Multiplier* as encoded by BA (groups of 2)
- Leave *Multiplicand* as is

Booth's multiplication algorithm is a multiplication algorithm that multiplies two signed binary numbers in two's complement notation. The algorithm was invented by Andrew Donald Booth in 1950 while doing research on crystallography at Birkbeck College in Bloomsbury, London. Booth's

Binary Multiplication

COMP122

Signed 2'sC Multiplication

Booth's multiplication algorithm

Booth's Recoding

From Wikipedia, the free encyclopedia

Booth's multiplication algorithm is a [multiplication algorithm](#) that multiplies two signed [binary](#) numbers in [two's complement notation](#). The [algorithm](#) was invented by [Andrew Donald Booth](#) in 1950 while doing research on [crystallography](#) at [Birkbeck College](#) in [Bloomsbury, London](#).^[1] Booth's algorithm is of interest in the study of [computer architecture](#).

The algorithm [\[edit \]](#)

Booth's algorithm examines adjacent pairs of [bits](#) of the 'N'-bit multiplier *Y* in signed [two's complement](#) representation, including an implicit bit below the [least significant bit](#), $y_{-1} = 0$. For each bit y_i , for i running from 0 to $N - 1$, the bits y_i and y_{i-1} are considered. Where these two bits are equal, the product accumulator *P* is left unchanged. Where $y_i = 0$ and $y_{i-1} = 1$, the multiplicand times 2^i is added to *P*; and where $y_i = 1$ and $y_{i-1} = 0$, the multiplicand times 2^i is subtracted from *P*. The final value of *P* is the signed product.

The representations of the multiplicand and product are not specified; typically, these are both also in two's complement representation, like the multiplier, but any number system that supports addition and subtraction will work as well. As stated here, the order of the steps is not determined. Typically, it proceeds from [LSB](#) to [MSB](#), starting at $i = 0$; the multiplication by 2^i is then typically replaced by incremental shifting of the *P* accumulator to the right between steps; low bits can be shifted out, and subsequent additions and subtractions can then be done just on the highest *N* bits of *P*.^[2] There are many variations and optimizations on these details.

The algorithm is often described as converting strings of 1s in the multiplier to a high-order +1 and a low-order -1 at the ends of the string. When a string runs through the MSB, there is no high-order +1, and the net effect is interpretation as a negative of the appropriate value.

1-strings

$$0111..1 = 1000..0 - 1$$

Binary Multiplication

Signed 2'sC Multiplication

Drobman MS Thesis

Booth's Recoding

y_{i+1}	y_i	y_{i-1}	y_{i+1}^*	y_i^*	M_i	Operation
0	0	0	0	0	0	add 0
0	0	1	0	1	1	add X
0	1	0	0	1	1	add X
0	1	1	1	0	2	add 2X
1	0	0	$\bar{1}$	0	2	subtract 2X
1	0	1	$\bar{1}$	1	$\bar{1}$	subtract X
1	1	0	0	$\bar{1}$	$\bar{1}$	subtract X
1	1	1	0	0	0	subtract 0

* bits recoded as a 1-string transformation

TABLE 2.1

Second-Order Recoding

Binary Multiplication



Signed 2'sC Multiplication

Booth's Recoding

Drobman MS Thesis
1973

UNIVERSITY OF CALIFORNIA

Los Angeles

Theory and Design of a
High Speed, Two's Complement Arithmetic Unit
Using an Array of Digital Multiplier Modules

A thesis submitted in partial satisfaction of the
requirements for the degree Master of Science
in Computer Science

by

Jeffrey Howard Drobman

Binary Multiplication

Signed 2'sC Multiplication

Drobman MS Thesis

2.3.2 Booth's Algorithm

Booth's Recoding

The discussion, so far, has been restricted to multipliers in magnitude representation. The concepts developed can be extended, however, to multipliers in two's complement as well. In fact, a simple recoding scheme for two's complement multipliers was developed some time ago by A. D. Booth and K. H. V. Booth, as described in Chu [6]. Booth's Algorithm (as it is commonly called) involves a recoding of the type described in the previous section with $k = 1$, with the important exception that when the most significant bit is a member of a 1-string, the multiplier is not extended -- due to its being in two's complement. Ignoring this extension preserves implicit value for two's complement multipliers, quite unlike the case of its magnitude representation.)

Booth's Algorithm is merely the recoding scheme itself, and Chu's presentation [6] starts with the recoding scheme and then works back to the original expression. While this does prove Booth's Al-

Am2505 Multiplier

Bit-slice 1971-80


18 SN 7437 N
604
N 7400A Sig.
DM 7400N Not.
M
F

Distinctive Characteristics:

- Provides 2's complement multiplication at high speed without correction.
- Can be used in an iterative scheme or time sequenced mode.
- Multiplies two 12-bit signed numbers in typically 200ns.

Am2505

 Four-Bit by Two-Bit 2's Complement Multiplier
Advanced Micro Devices
Complex Digital Integrated Circuits



- Multiplies in active HIGH (positive logic) or active LOW (negative logic) representations.
- Easy correction for unsigned, sign-magnitude or 1's complement multiplication.
- 100% reliability assurance testing in compliance with MIL STD 883.


FUNCTIONAL DESCRIPTION:

The Am2505 is a high-speed digital multiplier that can multiply numbers represented in the 2's complement notation and produce a 2's complement product without correction. The device consists of a 4x2 multiplier that can be connected to form iterative arrays able to multiply numbers either directly, or in a time sequenced arrangement. The device assumes that the most significant digit in a word carries a negative weight, and can therefore be used in arrays where the multiplicand and multiplier have different word lengths. The multiplier uses the quaternary algorithm and performs the function $S = XY + K$ where K is the input field used to add partial products generated in the array. At the beginning of the array the K inputs are available to add a signed constant to the least significant part of the product. Multiplication of an m bit number by an n bit number in an array results in a product having $m+n$ bits so that all possible combinations of product are accounted for. If a conventional 2's complement product is required the most significant bit can be ignored, and overflow conditions can be detected by comparing the last two product digits.

Figure 2 shows how multipliers are connected together in an array. A number of connection schemes are possible. Figure 4 shows diagrammatically the connection scheme that results in the fastest multiply. If higher speed is required an array can be split into several parts, and the parts added with high-speed look-ahead carry adders such as the Am9340.

Provision is made in the design for multiplication in the active high (positive logic) or active low (negative logic) representations simply by reinterpreting the active level of the input operands, the product, and a polarity control P . For a more complete description and applications the user is referred to the Am2505 Application Note.


LOGIC SYMBOLS

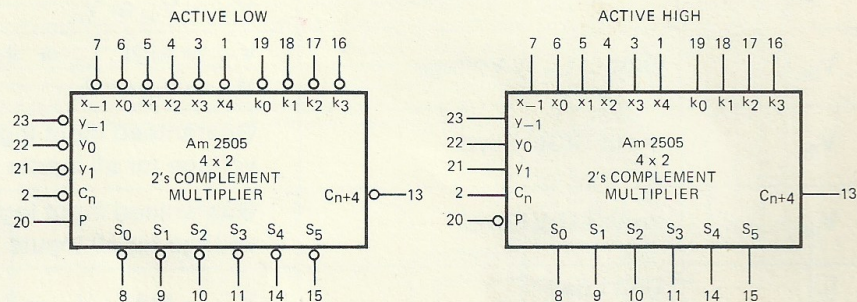

V_{CC} = PIN 24
GND = PIN 12

Am2505 Multiplier

Bit-slice 1971-80

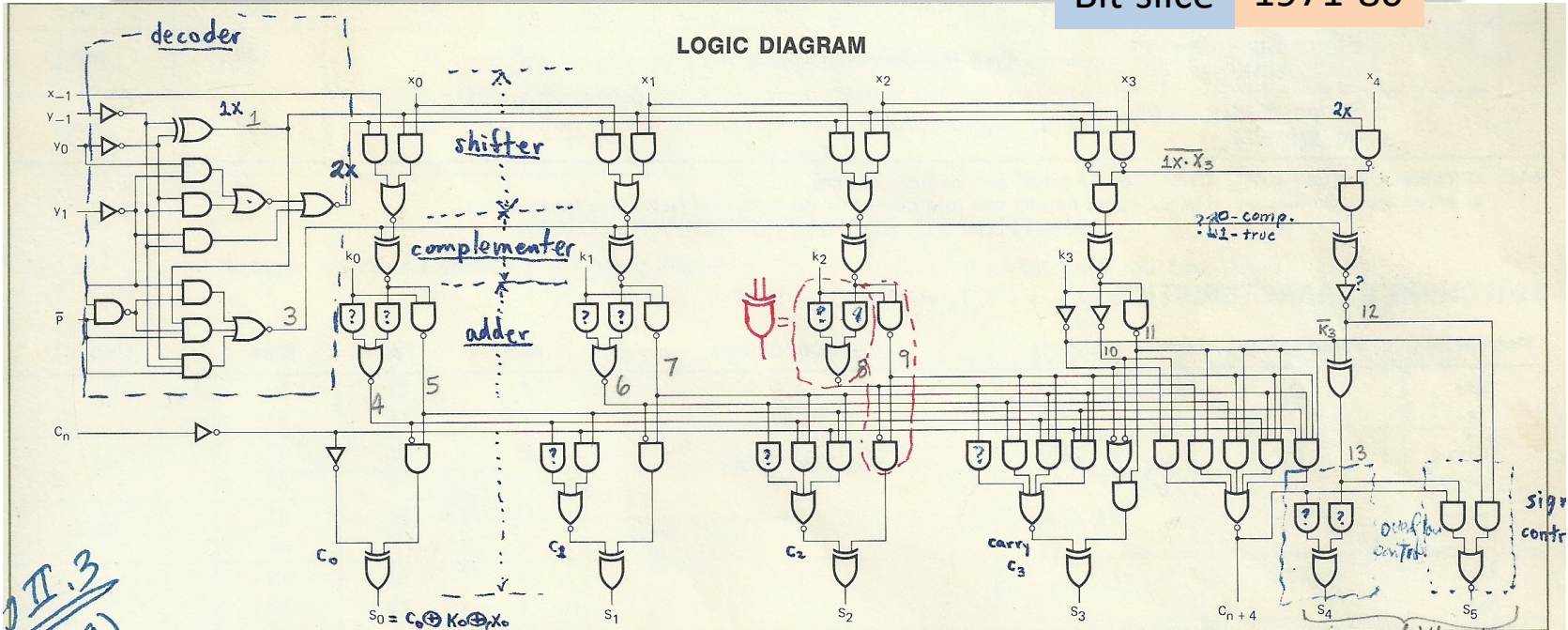

*Fig II.3
use #8
P.3*


Am2505 ORDERING INFORMATION

Package Type	Temperature Range	Order Number
Silicone DIP	0°C to +75°C	AM250559C
Hermetic DIP	0°C to +75°C	AM250559F
Hermetic DIP	-55°C to +125°C	AM250551F
Hermetic Flat Pak	-55°C to +125°C	AM250551P
Dice	Note	AM2505XXD

Note: The dice supplied will contain units which meet both 0°C to +75°C and -55°C to +125°C temperature ranges.

Fig. II.1.

CONNECTION DIAGRAM Top View

 


NOTE: PIN 1 is marked for orientation.

*ignored iff not MS pin
logic card:
top plane:
bottom plane:*

$S_0 = (x_0 \oplus y_0) \oplus C_n$


Am2505 Multiplier

Drobman MS Thesis Bit-slice 1971-80

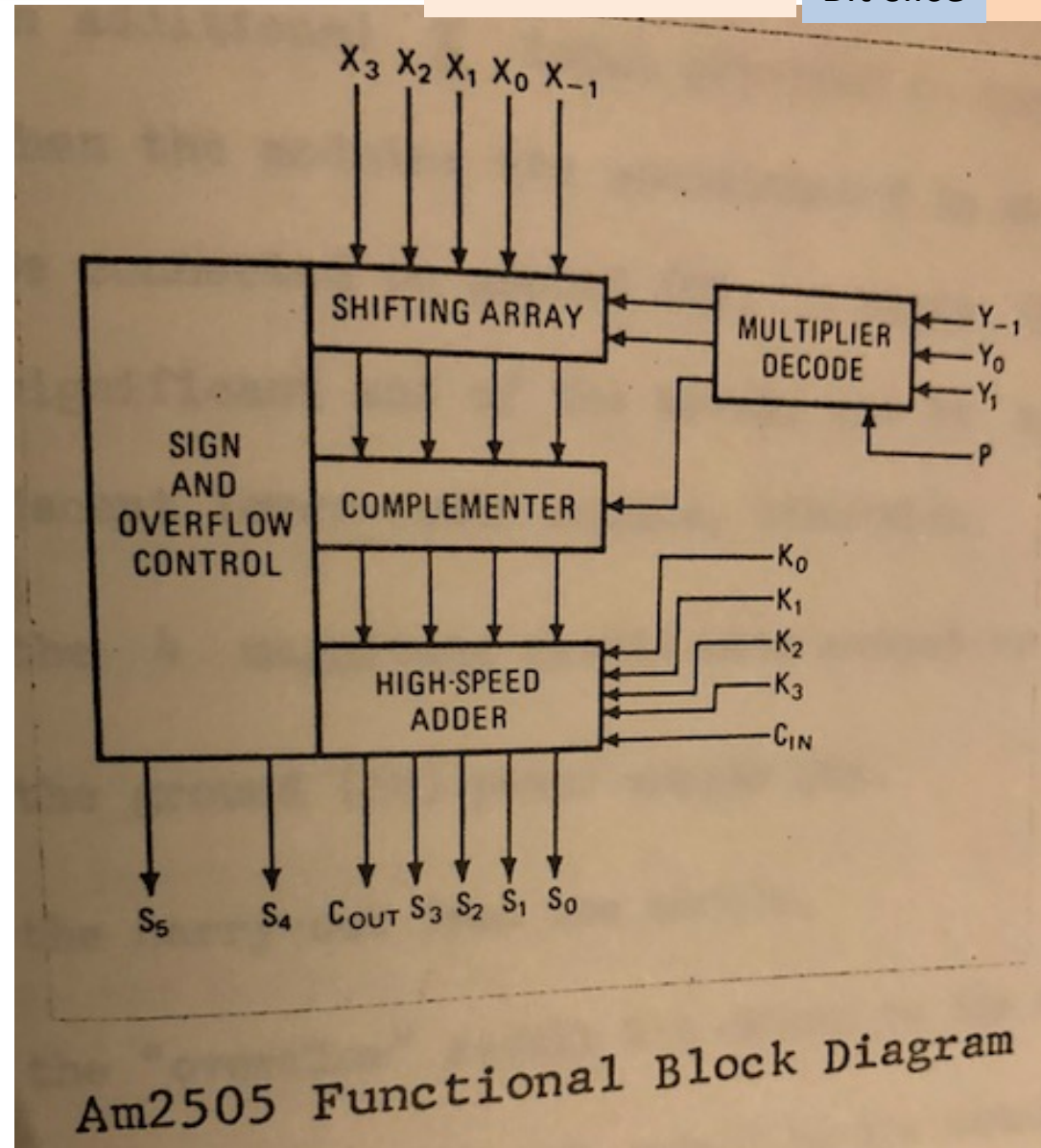

Am2505 Multiplier

Drobman MS Thesis Bit-slice 1971-80

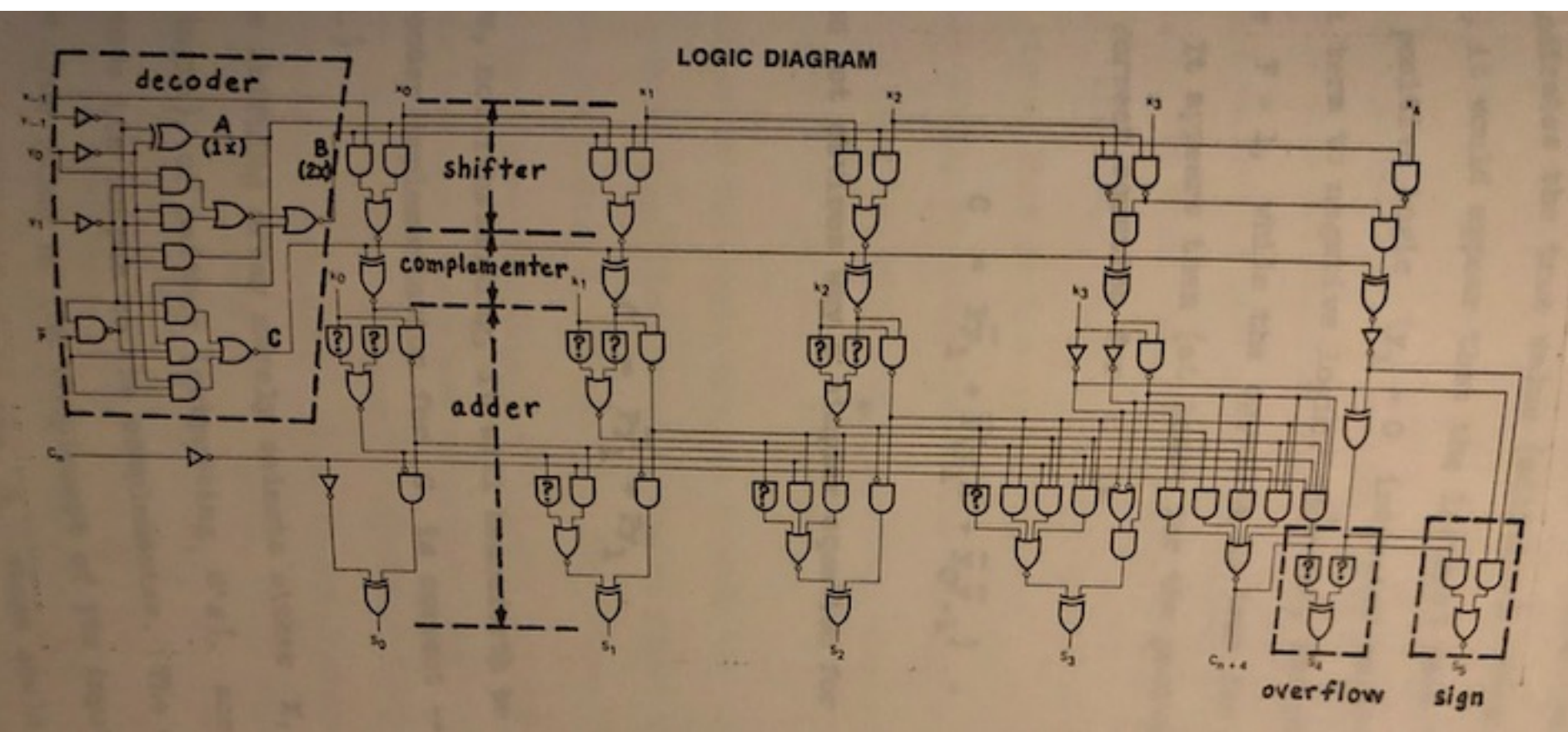

Am2505 Multiplier


Drobman MS Thesis Bit-slice 1971-80

Notation: (from [1], [15], [16])

multiplier pair = Y_{A+1}, Y_A

multiplicand group = $X_{B+3}, X_{B+2}, X_{B+1}, X_B$

"module designator" = (A,B)

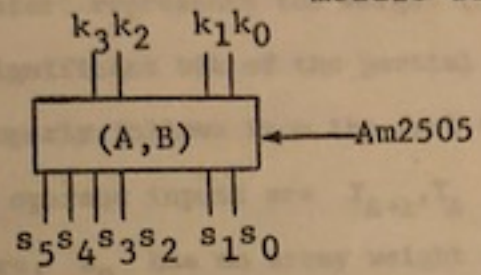

2x4-bit slices



8-bit x 8-bit multiply

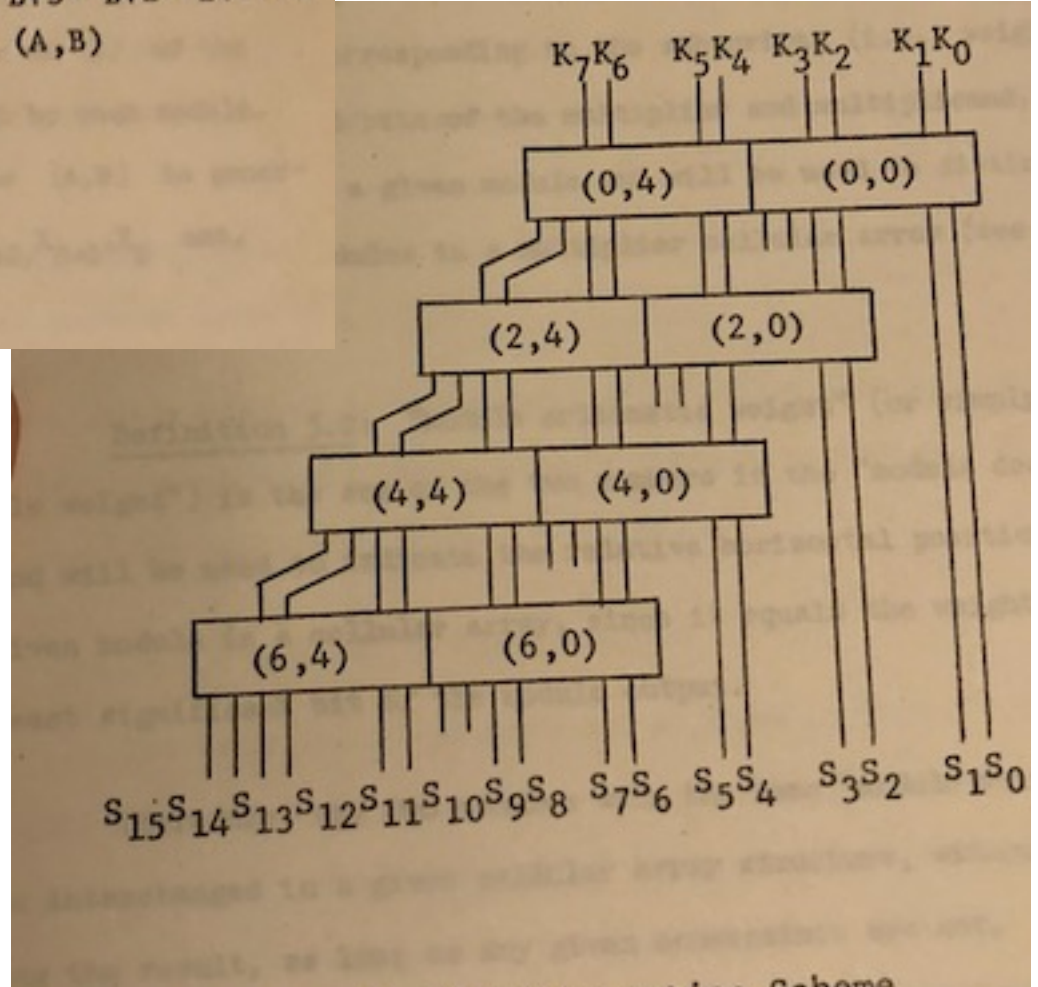


Figure 3.1. Basic Interconnection Scheme

Am2505 Multiplier

Timing Analysis

Drobman MS Thesis

Bit-slice

1971-80

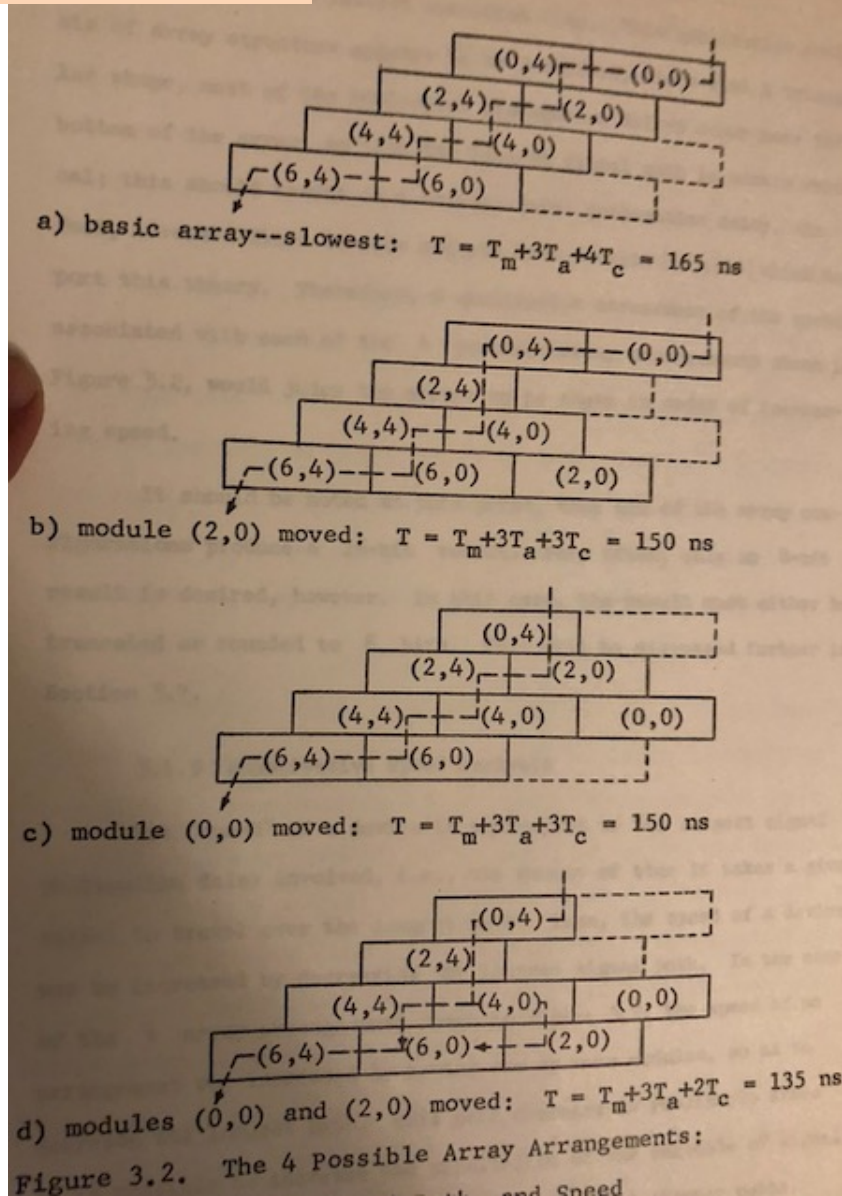


Figure 3.2. The 4 Possible Array Arrangements:

How do calculators calculate binary division?



Jeff Drobman, Lecturer at California State University, Northridge (2016-present)

Answered just now

the most common division algorithm used in the past was "non-restoring". but there are others, as listed in Wikipedia:

"Division algorithms fall into two main categories: slow division and fast division. Slow division algorithms produce one digit of the final quotient per iteration. Examples of slow division include [restoring](#) [↗](#), non-performing restoring, [non-restoring](#) [↗](#), and [SRT](#) [↗](#) division. Fast division methods start with a close approximation to the final quotient and produce twice as many digits of the final quotient on each iteration. [Newton-Raphson](#) [↗](#) and [Goldschmidt](#) [↗](#) algorithms fall into this category."

Division

Simple

Here's one way to implement the iterative approach: (There are [others...](#)) ↗

1. Align the leading 1s of the *significands*. ↗ This is usually easy in floating point—they're already aligned by the format, unless one or both of the numbers is *subnormal (aka. denormal)*. ↗
2. Compare the dividend and the divisor.
 - a. If the dividend is not smaller than the divisor, subtract the divisor from the dividend and write a 1.
 - b. Otherwise, don't subtract, and write a 0.
3. Shift the dividend (or what remains of it) left by 1 bit.
4. Repeat steps 2 and 3 until you have sufficient quotient bits—namely, that you have a 1 in the “hidden 1” position of the quotient.

Division

The original Pentium implemented a faster iterative approach that produced 2 bits per iteration: [Radix-4 SRT division](#). [↗](#) I won't go into the details of the algorithm. I will point out three salient features:




1. It recodes the numbers into a *redundant representation*, meaning that each bit of the inputs expand to multiple bits in the recoded representation. The redundant representation allows deferring carries and borrows.
2. It uses a large lookup table to decide what action to take at each step.
3. Rather than just producing 2 bits of quotient per iteration, it actually produces one of 5 values at each step: -2, -1, 0, +1, +2. Later steps can refine errors introduced in earlier steps.

The infamous [Pentium FDIV bug](#) [↗](#) arose from the lookup table mentioned above: There were 5 missing +2 entries in the lookup table on the buggy versions of the Pentium.

SRT division is a nice speedup, but it's only a linear speedup. That is, it doubles the speed. Double precision is still around twice as expensive as single precision.

Division

As transistors have gotten cheaper, modern hardware has turned to even faster approaches:


- [Newton-Raphson division](#)  works by iterating Newton's root-finding method on $f(x) = \frac{1}{x} - d$ to find the reciprocal of the divisor d . Once you find that, you multiply the dividend by that reciprocal. [The infamous Quake 3 Hack](#)  is based on this approach, although in that case it was inverse square root rather than an ordinary divide.
- [Goldschmidt division](#)  works a little differently. Multiply both dividend and divisor by a common factor F . F is chosen to push the divisor toward 1.0. Repeat until the divisor is close enough to 1, and stop. If you choose the common factor properly, this converges quickly. AMD processors since Athlon use this approach.

What's neat about Newton-Raphson and Goldschmidt approaches is that both converge *quadratically* when implemented properly. That is, each iteration doubles the number of valid bits in the result estimate. That means single precision results come after just a few iterations, and double precision computations usually only require one additional iteration.

Logic Timing

- Am2900
 - ❖ Combinational
 - Prop delays
 - ❖ Sequential
 - Setup times
 - Hold times

Sync Timing (AC)

 


Timing – Cycle Times

Am2900

MINIMUM CYCLE TIME CALCULATIONS FOR 16-BIT SYSTEMS

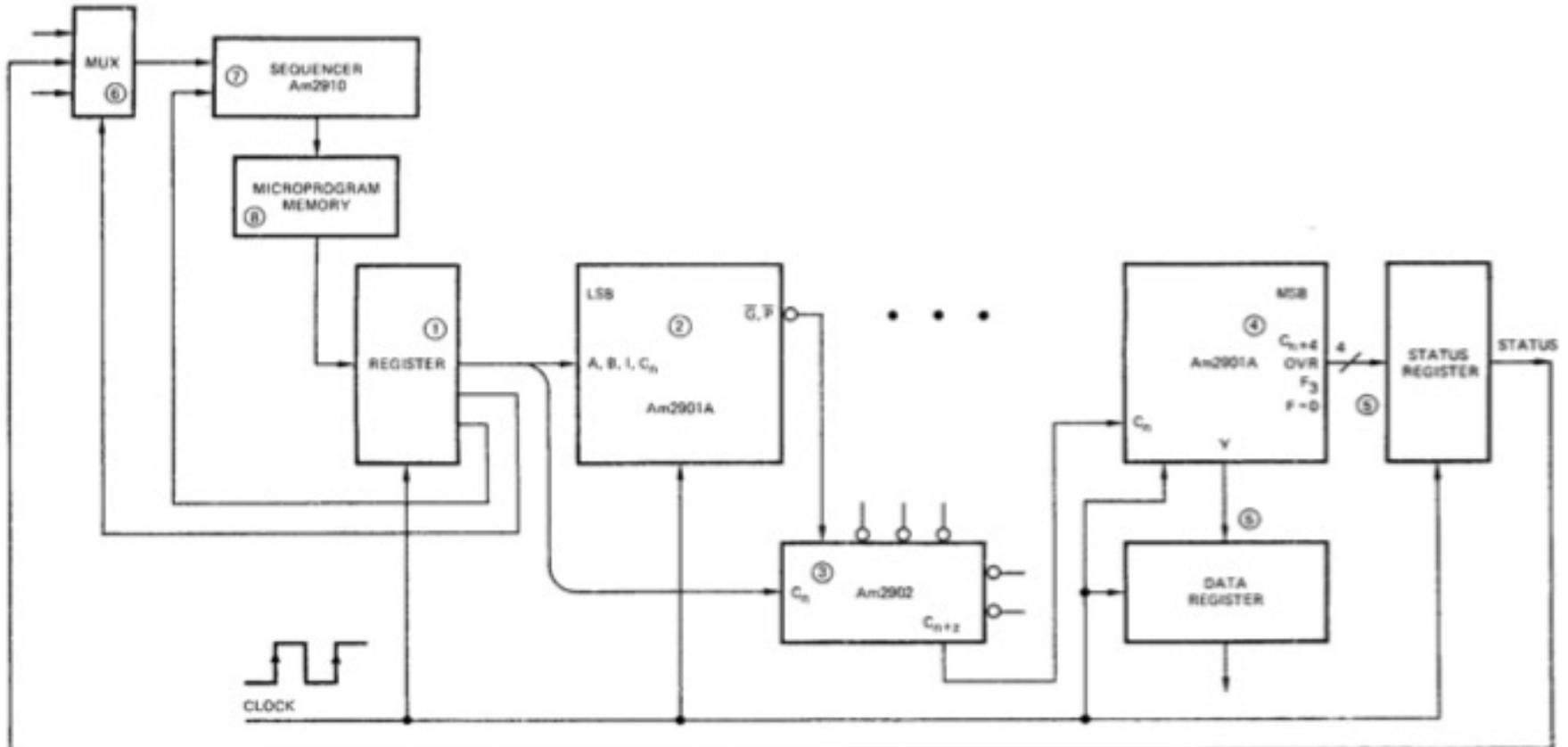Speeds used in calculations for parts other than Am2901B are representative for available MSI parts.



Timing

Am2900

B. Combinational Propagation Delays.
 $C_L = 50\text{pF}$

To Output From Input	Y	F3	Cn+4	$\overline{G}, \overline{P}$	F=0	OVR	RAM0 RAM3	Q0 Q3
A, B Address	60	61	59	50	70	67	71	–
D	38	36	40	33	48	44	45	–
Cn	30	29	20	–	37	29	38	–
I012	50	47	45	45	56	53	57	–
I345	51	52	52	45	60	49	53	–
I678	28	–	–	–	–	–	27	27
A Bypass ALU (I = 2XX)	37	–	–	–	–	–	–	–
Clock	49	48	47	37	58	55	59	29

C. Set-up and Hold Times Relative to Clock (CP) Input.

Input	CP:			
	Set-up Time Before H → L	Hold Time After H → L	Set-up Time Before L → H	Hold Time After L → H
A, B Source Address	20	0 (Note 3)	69 (Note 4)	0
B Destination Address	15	Do Not Change		0
D	–	–	51	0
Cn	–	–	39	0
I012	–	–	56	0
I345	–	–	55	0
I678	11	Do Not Change		0
RAM0, 3, Q0, 3	–	–	16	0

Timing – Logic

Am2900

TABLE IV E-2
 Guaranteed Combinational Delays
 $T_C = -55^\circ\text{C to } +125^\circ\text{C}, V_{CC} = 4.5\text{V to } 5.5\text{V}$
 Two's Complement Multiply Instruction
 ($I_{8765} = 2_H, I_{4321} = 0_H, I_0 = 0$)

To Output From Input	Slice Position	Y	C_{n+4}	$\overline{G}, \overline{P}$	Z (s)	N	OVR	DB	$\overline{\text{WRITE}}$	Q_{IO_0} Q_{IO_3}	S_{IO_0}	S_{IO_3}	S_{IO_0} Parity
A, B Address (Arith. Mode)	MSS	113	93	-	-	102	118	52	-	-	97	-	-
	IS, LSS	101	93	84	-	-	-	52	-	-	97	-	-
DA, DB Inputs	MSS	78	62	-	-	66	94	-	-	-	64	-	-
	IS, LSS	64	62	51	-	-	-	-	-	-	64	-	-
\overline{EA}	MSS	85	56	-	-	60	87	-	-	-	58	-	-
	IS, LSS	60	56	43	-	-	-	-	-	-	58	-	-
C_n	MSS	58	30	-	-	40	59	-	-	-	38	-	-
	IS, LSS	40	30	-	-	-	-	-	-	-	38	-	-
I_0	MSS	105	97	-	-	89	102	-	-	*	71*	*	-
	IS	105	97	81	-	-	-	-	-	*	71*	*	-
	LSS	105	97	81	42	-	-	-	53	*	71*	*	-
I_{4321}	MSS	112	98	-	-	94	111	-	-	*	75*	*	-
	IS	112	98	85	-	-	-	-	-	*	75*	*	-
	LSS	112	98	85	43	-	-	-	53	*	75*	*	-
I_{8765}	MSS	99	86	-	-	78	100	-	-	*	74*	*	-
	IS	99	86	84	-	-	-	-	-	*	74*	*	-
	LSS	99	86	84	48	-	-	-	50	*	74*	*	-
Clock	MSS	107	90	-	-	89	116	39	-	42	91	-	-
	IS, LSS	89	90	74	57	-	-	39	-	42	91	-	-
Z	MSS	90	65	-	-	70	81	-	-	-	72	-	-
	IS	90	65	48	-	-	-	-	-	-	72	-	-
\overline{IEN}	Any	-	-	-	-	-	-	-	24	-	-	-	-
S_{IO_3}, S_{IO_0}	Any	26	-	-	-	-	-	-	-	-	-	-	-

$F = S + C_n$ if $Z = 0$
 $S + R + C_n$ is $Z = 1$
 $Y_3 = F_3 \oplus OVR$ (MSS)
 $Z = Q_0$ (LSS)

Timing – Clocked

Am2900

TABLE IV B
Guaranteed Set-up and Hold Times
 $T_C = -55^{\circ}\text{C to } +125^{\circ}\text{C}, V_{CC} = 4.5\text{V to } 5.5\text{V}$
All Functions

CAUTION: READ NOTES TO TABLE B. NA = Not Applicable; no timing constraint.

Input	With Respect to this Signal	HIGH-to-LOW		LOW-to-HIGH		Comment
		Set-up	Hold	Set-up	Hold	
Y	Clock	NA	NA	23	3	To store Y in RAM or Q
$\overline{\text{WE}}$ HIGH	Clock	25	Note 2	Note 2	0	To Prevent Writing
$\overline{\text{WE}}$ LOW	Clock	NA	NA	35	0	To Write into RAM
A, B as Sources	Clock	38	3	NA	NA	See Note 3
B as a Destination	Clock and $\overline{\text{WE}}$ both LOW	6	Note 4	Note 4	3	To Write Data only into the Correct B Address
$\text{QIO}_0, \text{QIO}_3$	Clock	NA	NA	23	3	To Shift Q
I_{8765}	Clock	24	Note 5	Note 5	0	
$\overline{\text{IEN}}$ HIGH	Clock	30	Note 2	Note 2	0	To Prevent Writing into Q
$\overline{\text{IEN}}$ LOW	Clock	NA	NA	30	0	To Write into Q
I_{43210}	Clock	24	-	74	0	See Note 6

Notes:

- For set-up times from all inputs not specified in Table IV B, the set-up time is computed by calculating the delay to stable Y outputs and then allowing the Y set-up time. Even if the RAM is not being loaded, the Y set-up time is necessary to set-up the Q register. All unspecified hold times are less than or equal to zero relative to the clock LOW-to-HIGH edge.
- $\overline{\text{WE}}$ controls writing into the RAM. $\overline{\text{IEN}}$ controls writing into Q and, indirectly, controls $\overline{\text{WE}}$ through the write output. To prevent writing, $\overline{\text{IEN}}$ and $\overline{\text{WE}}$ must be HIGH during the entire clock LOW time. They may go LOW after the clock has gone LOW to cause a write provided the $\overline{\text{WE}}$ LOW and $\overline{\text{IEN}}$ LOW set-up times are met. Having gone LOW, they should not be returned HIGH until after the clock has gone HIGH.
- A and B addresses must be set-up prior to clock LOW transition to capture data in latches at RAM output.
- Writing occurs when CP and $\overline{\text{WE}}$ are both LOW. The B address should be stable during this entire period.
- Because I_{8765} control the writing or not writing of data into RAM and Q, they should be stable during the entire clock LOW time unless $\overline{\text{IEN}}$ is HIGH, preventing writing.
- The set-up time prior to the clock LOW-to-HIGH transition occurs in parallel with the set-up time prior to the clock HIGH-to-LOW transition and the clock LOW time. The actual set-up time requirement on I_{43210} , relative to the clock LOW-to-HIGH transition, is the longer of (1) the set-up time prior to clock L → H, and (2) the sum of the set-up time prior to clock H → L and the clock LOW time.

Section



State Machines


FSM

State Machines

FSM

Figure 8.10.3: A finite-state machine is implemented with a state register that holds the current state and a combinational logic block to compute the next state and output functions (COD Figure B.10.3).

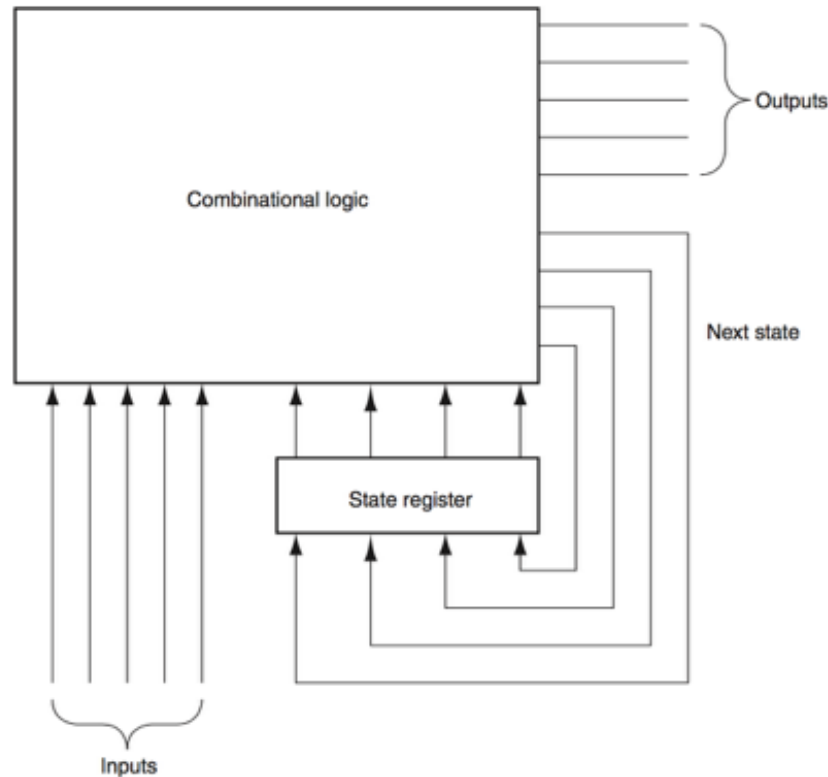The latter two functions are often split apart and implemented with two separate blocks of logic, which may require fewer gates.



Section



Computer Logic Boards

DG Nova 16-bit Mini Circuit

COMP122

4x TI '181 4-bit ALU slice

